

Digital Logic design 901220

By: Dr. Wa'el Al Qassas
Al Albayt university

Text Book : Digital Logic & Computer Design/Moris Mano
Course part

- Theoretical Lectures: 3 hours weekly
- Practical LAB: 1 lab (2 hours) weekly

Grading policy:

- First Theoretical Exam: 15 points
- Second Theoretical Exam: 15 points
- Final Theoretical Exam : 40 points
- Mid Practical Exam: 10 points
- Final Practical Exam: 10 points

Web sites.

[Www.geocities.com/wael it2003](http://www.geocities.com/wael_it2003)

www.aabu.edu.jo/it/~wael

<http://web2.aabu.edu.jo:8080>

[http://web2.aabu.edu.jo:8080/tool/course file/
901220_lectures.pdf](http://web2.aabu.edu.jo:8080/tool/course_file/901220_lectures.pdf)

www.aabu.edu.jo/~wael

Syllabus

- Syllabus review & Introduction :1 hour
- Simple logic Circuits and manufacturing technology :1 hours
- Truth table and symbolic representation :1 hour
- Fundamental properties for Boolean algebra :1 hours
- Implementing Circuits form Truth table , practice : 2 hours
- XOR gate, Demorgan's Law : 1 hour
- Logical expression simplification using Fundamental properties, Demorgan , Practice : 1 hours.
- Karnaugh map (3 input, 4 input), SOP,POS, practice: 3 hour
- Tabulation method : 2 hours.
- Numbering systems, Binary numbers, Hexadecimal,..., real number implementation,: 3 hours
- First exam., Question solving & evaluation : 1 hour.

Transistor: Building Block of Computers

Microprocessors contain millions of transistors

- Intel Pentium II: **7 million**
- Compaq Alpha 21264: **15 million**
- Intel Pentium III: **28 million**

Logically, each transistor acts as a switch

Combined to implement logic functions

- AND, OR, NOT

Combined to build higher-level structures

- Adder, multiplexer, decoder, register, ...

5

وائل قصاص/AABU


Simple Switch Circuit

Switch **open**:

- No current through circuit
- Light is **off**
- V_{out} is **+5V**

Switch **closed**:

 - Short circuit across switch
- Current flows
- Light is **on**
- V_{out} is **0V**




Switch-based circuits can easily represent two states:
on/off, open/closed, voltage/no voltage.

6

وائل قصاص/AABU

LOGICAL AND:

 

7

وائل قصاص/AABU


N-type MOS Transistor

MOS = Metal Oxide Semiconductor

- two types: N-type and P-type

N-type

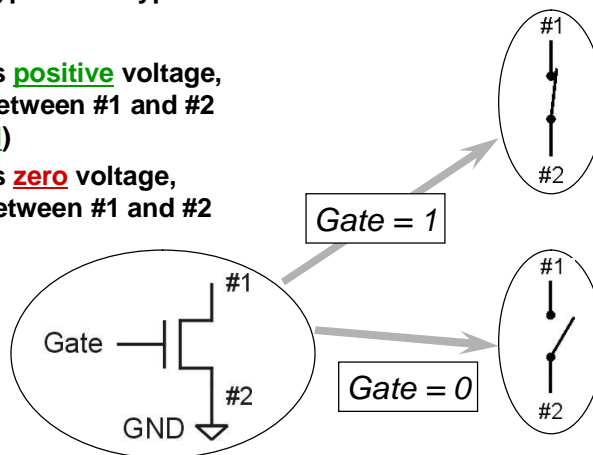- when Gate has **positive** voltage, short circuit between #1 and #2 (switch **closed**)
- when Gate has **zero** voltage, open circuit between #1 and #2 (switch **open**)



Terminal #2 must be connected to GND (0V).


8

وائل قصاص/AABU

P-type MOS Transistor

P-type is *complementary* to N-type

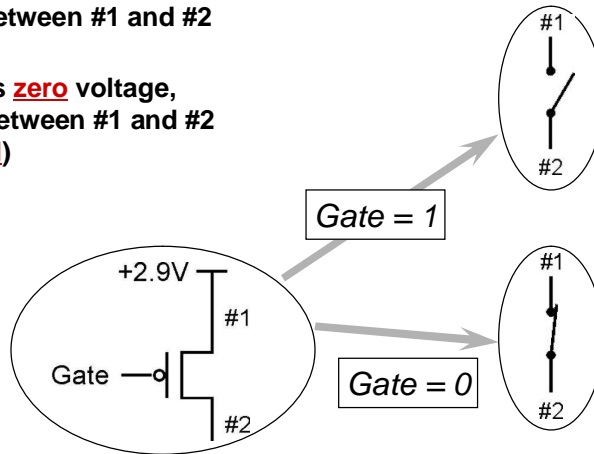- when Gate has **positive** voltage, open circuit between #1 and #2 (switch **open**)
- when Gate has **zero** voltage, short circuit between #1 and #2 (switch **closed**)



Terminal #1 must be connected to +2.9V.

9


وائل قصاص/AABU

Logic Gates

Use switch behavior of MOS transistors to implement logical functions: AND, OR, NOT.

Digital symbols:

 - recall that we assign a range of analog voltages to each digital (logic) symbol






- assignment of voltage ranges depends on electrical properties of transistors being used
 - Ø typical values for "1": +5V, +3.3V, +2.9V
 - Ø from now on we'll use +5V

10

وائل قصاص/AABU

Inverter (NOT Gate)

   



Truth table

In	Out	In	Out
0 V	2.9 V	0	1
2.9 V	0 V	1	0

11

وائل قصاص/AABU

NOR Gate

  


A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

Note: Serial structure on top, parallel on bottom.

12

وائل قصاص/AABU

OR Gate

 



A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

Add inverter to NOR.

13

وائل قصاص/AABU

NAND Gate (AND-NOT)

  


A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Note: Parallel structure on top, serial on bottom.

14

وائل قصاص/AABU

AND Gate

 


A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

Add inverter to NAND.


15

وائل قصاص/AABU


Basic Logic Gates

 

NOT

 


OR

 

NOR



AND

 

NAND

16

وائل قصاص/AABU

Fundamental Properties of boolean algebra:

Commutative:

$$\emptyset X + Y = Y + X$$

$$\emptyset X \cdot Y = Y \cdot X$$

Associative:

$$\emptyset (X + Y) + Z = X + (Y + Z)$$

$$\emptyset (X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$$

Identity:

$$\emptyset X + 0 = X$$

$$\emptyset X \cdot 1 = X$$

Complement:

$$\emptyset X + (X') = 1$$

$$\emptyset X \cdot (X') = 0$$

Distributive:

$$\emptyset X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$$

$$\emptyset X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$$

Absorption

$$\emptyset X + X \cdot Y = X$$

$$X \cdot X = X$$

$$X + X = X$$

$$X + 1 = 1$$

$$X \cdot 0 = 0$$

$$X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$$

X Y Z	Y+Z	X.(Y+Z)	X.Y	X.Z	(X.Y)+(X.Z)
0 0 0	0	0	0	0	0
0 0 1	1	0	0	0	0
0 1 0	1	0	0	0	0
0 1 1	1	0	0	0	0
1 0 0	0	0	0	0	0
1 0 1	1	1	0	1	1
1 1 0	1	1	1	0	1
1 1 1	1	1	1	1	1

19

وانئل قضااص/AABU

$$X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$$

X Y Z	Y.Z	X+(Y.Z)	X+Y	X+Z	(X+Y).(X+Z)
0 0 0	0	0	0	0	0
0 0 1	0	0	0	1	0
0 1 0	0	0	1	0	0
0 1 1	1	1	1	1	1
1 0 0	0	1	1	1	1
1 0 1	0	1	1	1	1
1 1 0	0	1	1	1	1
1 1 1	1	1	1	1	1

20


وانئل قضااص/AABU

More than 2 Inputs?

AND/OR can take any number of inputs.

- AND = 1 if all inputs are 1.
- OR = 1 if any input is 1.
- Similar for NAND/NOR.

 Can implement with multiple two-input gates,
or with single CMOS circuit.



21

وانئل قضااص/AABU

Practice

Implement a 3-input NOR gate with CMOS.


22

وانئل قضااص/AABU

Logical Completeness

Can implement ANY truth table with AND, OR, NOT.

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 

1. AND combinations that yield a "1" in the truth table.

2. OR the results of the AND gates.


23

وائل قصاص/AABU

Practice

Implement the following truth table.

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

 

24

وائل قصاص/AABU


Another example:

We want to build a circuit that has 3 binary inputs.

This CKT is On if the inputs are $X'Y'Z$ or $X'YZ'$.

Build the Truth table, then Draw the Ckt

X	Y	Z	Output
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

 


25

وائل قصاص/AABU


XOR gate:

$$A \text{ XOR } B = A \cdot B' + A' \cdot B$$

$$A \oplus B$$

 

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

 


26

وائل قصاص/AABU

DeMorgan's Law

Converting AND to OR (with some help from NOT)

Consider the following gate:

 

A	B	\bar{A}	\bar{B}	$\bar{A} \cdot \bar{B}$	$\overline{\bar{A} \cdot \bar{B}}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

To convert AND to OR
(or vice versa),
invert inputs and output.

Same as A+B!

27

وائل قصاص/AABU

DeMorgan Law:

$$\overline{A+B} = (\bar{A} \cdot \bar{B})'$$

A	B	A'	B'	A'.B'	(A'.B')'
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

OR
Truth
table

$$\overline{A \cdot B} = (A'+B)'$$

A	B	A'	B'	A'+B'	(A'+B')'
0	0	1	1	1	0
0	1	1	0	1	0
1	0	0	1	1	0
1	1	0	0	0	1

AND
Truth
table

28

وائل قصاص/AABU

Build the following logical expression using AND, Not Gates only:

$$\begin{aligned} F &= X \cdot Y + Z' \\ &= ((X \cdot Y)' \cdot Z'')' \\ &= ((X \cdot Y)' \cdot Z)' \end{aligned}$$

Another example:

$$\begin{aligned} F &= XYZ + Y'Z + XZ' \\ &= ((XYZ)' \cdot (Y'Z)' \cdot (XZ')')' \end{aligned}$$

Simplify the following boolean expression

$$\begin{aligned} F &= (A'BC \oplus C + A + D)' \\ &= (A'BCC' + (A'BC)'C + A + D)' \\ &= (0 + (A'BC)'C + A + D)' \\ &= (0 + (A+B'+C')C + A + D)' \\ &= (AC + B'C + C'C + A + D)' \\ &= (AC + B'C + 0 + A + D)' \\ &= (AC + A + B'C + D)' \\ &= (A + B'C + D)' \\ &= A' (B'C)' D' \\ &= A' D' (B + C') \\ &= A'BD' + A'C'D' \end{aligned}$$

Simplification using boolean algebra:

We have the following truth table for a logical circuit and we want to implement this using the minimum number of gates:

SOP

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$\begin{aligned}
 F &= A'B'C + A'BC + AB'C' + AB'C + ABC' \\
 &= A'B'C + A'BC + AB'(C+C') + ABC' \\
 &= A'C(B+B') + AB' + ABC' \\
 &= A'C + AB' + AC'(B+B') ; \text{we can reuse } AB'C' \\
 &= A'C + AB' + AC'
 \end{aligned}$$

31

وانئل قضااص/AABU

Another example:

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$\begin{aligned}
 F &= A'B'C + A'BC + AB'C + ABC' + ABC \\
 &= A'C(B+B') + AB'C + ABC' + ABC \\
 &= A'C + AC(B'+B) + ABC' \\
 &= A'C + AC + AB(C+C') \\
 &= A'C + AC + AB \\
 &= C(A+A') + AB \\
 &= C + AB
 \end{aligned}$$

32

وانئل قضااص/AABU

Karnaugh Maps

Karnaugh map : is a representation for the truth table in a graphical way, which makes the simplification of any boolean function easier.

For 3 input boolean function the Karnaugh map will be as follows :

		BC			
		00	01	11	10
A	0	A'B'C' 000	A'B'C 001	A'BC 011	A'BC' 010
	1	AB'C' 100	AB'C 101	ABC 111	ABC' 110

As we can see, each cell represent one row of the truth table

Next step is to fill the map using the truth table output.

33

وانئل قضااص/AABU

Simplification using Karnaugh:

Let us resolve the previous examples using karnaugh map:

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

		BC			
		00	01	11	10
A	0	0	1	1	0
	1	1	1	0	1

$$F = A'C + AC' + B'C$$

34

وانئل قضااص/AABU

Resolve the same example in another way:

	BC			
	00	01	11	10
0	0	1	1	0
1	1	1	0	1

$$F = A'C + AB' + AC'$$

35

وانئل قضااص /AABU

Another example

	00	01	11	10
0	0	1	1	0
1	1	1	1	1

36

وانئل قضااص /AABU

Convert from logical expression to minterms

What are the minterms that represent the following expression assuming that we have 3 inputs A,B, and C

$$F=A+A'C$$

F=

37

وانئل قضااص/AABU

Karnaugh map for 4 input boolean function

		CD			
		00	01	11	10
AB	00	0 0000	1 0001	3 0011	2 0010
	01	4 0100	5 0101	7 0111	6 0110
	11	12 1100	13 1101	15 1111	14 1110
	10	8 1000	9 1001	11 1011	10 1010

38

وانئل قضااص/AABU

39
وائل قصاص / AABU

Assume we have the boolean function F with 4 inputs:
 $F(A,B,C,D) = \sum (0,1,4,6,8,11,13,15)$
Ø Make the truth table for this function
Ø Write the boolean equation for this function (Before simplification)
Ø Simplify this function using karnaugh map technique
Ø Draw the simplified equation.

	00	01	11	10
00	1	1		
01	1			1
11		1	1	
10	1		1	

40
وائل قصاص / AABU

Minterms & Maxterms

To understand the relation between Minterms and Maxterms let us see the following example:

$$F = \Sigma(1,3,5,6,7)$$

$$F = A'B'C + A'BC + AB'C + ABC' + ABC$$

$$F' = A'B'C' + A'BC' + AB'C'$$

We know that $F'' = F$

$$F = F'' = (A'B'C' + A'BC' + AB'C')'$$

$$F = (A'B'C')' \cdot (A'BC')' \cdot (AB'C')'$$

$$F = (A+B+C) \cdot (A+B'+C) \cdot (A'+B+C)$$

$$F = \Pi(0,2,4)$$

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

41

وانئل قضااص/AABU

Minterms & Maxterms

For a 3 binary variables

x y z	Minterms		Maxterms	
	Term	Designation	Term	Designation
0 0 0	$x'y'z'$	m_0	$x+y+z$	M_0
0 0 1	$x'y'z$	m_1	$x+y+z'$	M_1
0 1 0	$x'yz'$	m_2	$x+y'+z$	M_2
0 1 1	$x'yz$	m_3	$x+y'+z'$	M_3
1 0 0	$xy'z'$	m_4	$x'+y+z$	M_4
1 0 1	$xy'z$	m_5	$x'+y+z'$	M_5
1 1 0	xyz'	m_6	$x'+y'+z$	M_6
1 1 1	xyz	m_7	$x'+y'+z'$	M_7

42

وانئل قضااص/AABU

5 variables Karnaugh map

		CDE							
		000	001	011	010	110	111	101	100
AB	00								
	01								
	11								
	10								

43

وائل قصاص/AABU

Tabulation method

- Last lecture we noticed the difficulty of simplifying 5 variable equations using karnaugh Map.
- Another method is used to simplify boolean equations.
- Tabulation method (Quine-McCluskey), or prime implicants :-
 - Its suitable for machine computation
 - Uses two phases:
 - i. Finding Prime implicants
 - ii. Selecting Prime implicants

44

وائل قصاص/AABU

Determining Prime implicants

Example 1 : $F(w,x,y,z)=\Sigma(0,1,2,8,10,11,14,15)$

First we list the minterms in groups depending on the number of ones in each minterm

0 0000

~~~~~

1 0001

2 0010

8 1000

~~~~~

10 1010

~~~~~

11 1011

14 1110

~~~~~

15 1111

45

وانئل قصاص/AABU

Then look for any two minterms that differ on one variable only , between any adjacent groups

<u>0</u> 0000	0,1 000-	0,2,8,10 -0-0
1 0001	0,2 00-0	<u>0,8,2,10</u> -0-0
2 0010	<u>0,8</u> -000	10,11,14,15 1-1-
8 1000	2,10 -010	10,14,11,15 1-1-
<u>10</u> 1010	8,10 10-0	
11 1011	10,11 101-	
<u>14</u> 1110	<u>10,14</u> 1-10	
15 1111	11,15 1-11	
	14,15 111-	

The prime implicants are : $w'x'y'$, $x'z'$, wy

Next step is to select needed prime implicants.

46

وانئل قصاص/AABU

	0	1	2	8	10	11	14	15
W'X'Y'	V	V						
X'Z'	V		V	V	V			
WY					V	V	V	V

Example 2

Simplify the following SOP using tabulation method.

$$F(W,X,Y,Z)=\Sigma(1,4,6,7,8,9,10,11,15)$$

Remember : first Find Prime implicants

then select the needed prime implicants.

Determining the prime implicants

1	0001	1,9	-001	8,9,10,11	10- -
4	0100	4,6	01-0	8,10,9,11	10- -
8	1000	8,9	100-	~~~~~	
	~~~~~	8,10	10-0		
6	0110	~~~~~			
9	1001	6,7	011-		
10	1010	9,11	10-1		
	~~~~~	10,11	101-		
7	0111	~~~~~			
11	1011	7,15	-111		
	~~~~~	11,15	1-11		
15	1111				

$X'Y'Z, W'XZ', W'XY, XYZ, WYZ, WX'$

### • Selection for the needed prime implicants

	1	4	6	7	8	9	10	11	15
$X'Y'Z$	V					V			
$W'XZ'$		V	V						
$W'XY$			V	V					
$XYZ$				V					V
$WYZ$								V	V
$WX'$					V	V	V	V	

### IC's characteristics ( From Ch 1):

ØFan-out: the number of standard loads that the output of a gate can drive without impairing its normal operation ( 20 to 50 gates)

ØPower dissipation : the supplied power required to operate the gate ( in mW)

ØPropagation delay: The average transition delay time for a signal to propagate from input to output when the binary signals change in value ( in ns)

51

وانئل قصابص/AABU

### Binary numbers ( Chapter 1)

qComputers uses Binary system.

qWe need to represent different numbering types use the Binary system.

qRemember the conversion between Binary & Decimal, this was used to represent positive integer numbers only.

qBut , what about negative numbers.

qThree different methods were used to represent negative integer numbers:

qSign magnitude

qOnes Complement

qTwos complement

52

وانئل قصابص/AABU

## Binary numbers

53

وانئل قصابص/AABU

## Negative numbers (Sign magnitude)

This technique uses additional binary digit to represent the sign, 0 to represent positive, 1 to represent negative.

qEx.:

$$5 = 0101$$

$$-5 = 1101$$

Also

$$5 = 00000101$$

$$-5 = 10000101$$

[www.microcode.com](http://www.microcode.com) Circuit maker

54

وانئل قصابص/AABU

## Negative numbers (1's Complement)

q1's comp is another method used to represent negative numbers.

qIn this method we invert every bit in the positive number in order to represent its negative.

qEx.:

$$9 = 01001$$

$$-9 = 10110$$

qAgain remember that we use additional digit to represent the sign

qWe may represent 9 as 00001001 ; zeros on left have no value

-9 in 1's comp will be 11110110

55

وائل قصاص/AABU

## Negative numbers (2's complement)

qThis is the method which is used in most computers to represent integer numbers nowadays.

qRemember always to represent a positive number using any of the previous methods is the same, all what is needed is a 0 on the left to show that the number is positive

qTo represent a negative number in 2's Comp , first we find the 1's Comp, then add 1 to the result

qEx:

How we represent -9 in 2's comp

1- 9 in binary= 01001

2- invert = 10110

3 add 1 = 10111; -9 in 2's Comp.

56

وائل قصاص/AABU

**-22**

**22 = 010110**

**In 1's = 101001**

**In 2's = 101010 -22 in 2's comp**


57


وائل قصاص/AABU

### Two's Complement Shortcut

To take the two's complement of a number:

- copy bits from right to left until (and including) the first "1"
- flip remaining bits to the left

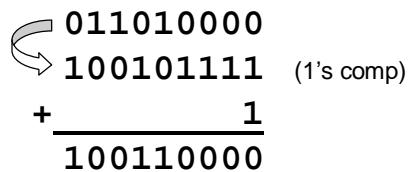  
011010000  
100101111 (1's comp)  
+                   1  
-----  
100110000

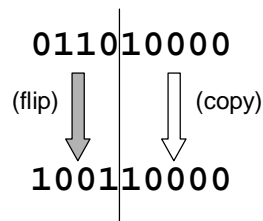  
0110|10000  
(flip) ↓        ↓ (copy)  
1001|10000

58

وائل قصاص/AABU

## Operations: Arithmetic and Logical

Recall:

a data type includes *representation* and *operations*.

We now have a good representation for signed integers, so let's look at some arithmetic operations:

- Addition
- Subtraction
- Sign Extension

We'll also look at overflow conditions for addition.

Multiplication, division, etc., can be built from these basic operations.

Logical operations are also useful:

- AND
- OR
- NOT

59

وائل قصاص/AABU

## Addition

As we've discussed, 2's comp. addition is just binary addition.

- assume all integers have the same number of bits
- ignore carry out
- for now, assume that sum fits in n-bit 2's comp. representation

$$\begin{array}{r} 01101000 \ (104) \\ + \underline{11110000} \ (-16) \\ \hline 01011000 \ (88) \end{array} \qquad \begin{array}{r} 11110110 \ (-10) \\ + \underline{\hspace{2cm}} \ (-9) \\ \hline \hspace{2cm} \ (-19) \end{array}$$

*Assuming 8-bit 2's complement numbers.*

60

وائل قصاص/AABU

## Subtraction

Negate subtrahend (2nd no.) and add.

- assume all integers have the same number of bits
- ignore carry out
- for now, assume that difference fits in n-bit 2's comp. representation

$$\begin{array}{r} 01101000 \text{ (104)} \\ - 00010000 \text{ (16)} \\ \hline 01101000 \text{ (104)} \\ + 11110000 \text{ (-16)} \\ \hline 01011000 \text{ (88)} \end{array} \qquad \begin{array}{r} 11110110 \text{ (-10)} \\ - \phantom{00000000} \text{ (-9)} \\ \hline 11110110 \text{ (-10)} \\ + \phantom{00000000} \text{ (9)} \\ \hline \phantom{01011000} \text{ (-1)} \end{array}$$

Assuming 8-bit 2's complement numbers.

61

وائل قصاص/AABU

## Sign Extension

To add two numbers, we must represent them with the same number of bits.

If we just pad with zeroes on the left:

<u>4-bit</u>	<u>8-bit</u>
0100 (4)	00000100 (still 4)
1100 (-4)	00001100 (12, not -4)

Instead, replicate the MS bit -- the sign bit:

<u>4-bit</u>	<u>8-bit</u>
0100 (4)	00000100 (still 4)
1100 (-4)	11111100 (still -4)

62

وائل قصاص/AABU

## Overflow

If operands are too big, then sum cannot be represented as an  $n$ -bit 2's comp number.

$$\begin{array}{r} 01000 \quad (8) \\ + \underline{01001} \quad (9) \\ \hline 10001 \quad (-15) \end{array} \qquad \begin{array}{r} 11000 \quad (-8) \\ + \underline{10111} \quad (-9) \\ \hline 01111 \quad (+15) \end{array}$$

We have overflow if:

- signs of both operands are the same, and
- sign of sum is different.

Another test -- easy for hardware:

- carry into MS bit does not equal carry out

63

وائل قصاص/AABU

## Build a Ckt that discovers the overflow

Inputs Sa: Sign for the first number

Sb: Sign for the second number

Ss: Sign for the answer number

Sa	Sb	Ss	Overflow
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

64

وائل قصاص/AABU



### Real numbers ( outside the text book)

qAll what we discussed before was about integers.

qWhat about real numbers (ex.: 6.125)

qTo represent real numbers we take first the integer part and convert it as we learned before, and then take the fraction part and convert it using the following algorithm

q 1- multiply fraction by 2

q 2- take the integer of the result

q 3- Repeat 1 and 2 until the fraction is zero, or until u reach get enough digits.

qEx. : 6.125

$$6 = 110$$

$$0.125 \times 2 = 0.25$$

$$0.25 \times 2 = 0.5$$

$$0.5 \times 2 = 1.0$$

$$6.125 = 110.001$$

Another example:

Convert 9.2 to binary.

$$9 = 1001$$

$$0.2 \times 2 = 0.4$$

$$0.4 \times 2 = 0.8$$

$$0.8 \times 2 = 1.6 ; \text{ take the fraction only}$$

$$0.6 \times 2 = 1.2$$

$$0.2 \times 2 = 0.4 ; \text{ let us stop here, 5 digits after the point}$$

The binary equivalent will be: 1001.00110

## Convert from binary

Again let us take the previous results

$$2^2 2^1 2^0 2^{-1} 2^{-2} 2^{-3}$$

$$1 1 0 . 0 0 1$$

$$= 4+2+.125=6.125$$

Ex. 2:

$$2^3 2^2 2^1 2^0 2^{-1} 2^{-2} 2^{-3} 2^{-4} 2^{-5}$$

$$1 0 0 1 . 0 0 1 1 0$$

$$= 8+1+ .125+.0625 = 9.1875$$

Why not 9.2 !??

67

وائل قصاص/AABU

## Floating numbers

Nowadays numbers with decimal point are represented in the computer using IEEE 754 float number format.

This format has to subtypes :

- Float: 32 bit number can represent up to  $10^{35}$ .
- Double: 64 bit number can represent up to  $10^{350}$  with more number of digits after the point.

We will not cover this topic here.

It will be covered in Computer architecture course.

68

وائل قصاص/AABU

## Hexadecimal

qAs we noticed to read a long binary number is confusing

qSo another numbering system was invented ( base 16)

qWe know base 10 ,base 2, and now base 16

qNumbers in (base 16) are : 0,1,2,3,4,5,6,7,8,9,A,B,C,D,E,F

qThere is a direct relation between base 2 and base 16,  
 $2^4=16$  , so the conversion from binary to hexadecimal is quite easy.

qEach 4 binary digits are converted to one hexadecimal digit.

69

وائل قصاص/AABU

Decimal	Binary	Hexadecimal
0	0000	0
1	0001	1
2	0010	2
3	0011	3
4	0100	4
5	0101	5
6	0110	6
7	0111	7
8	1000	8
9	1001	9
10	1010	A
11	1011	B
12	1100	C
13	1101	D
14	1110	E
15	1111	F

70

وائل قصاص/AABU

## Examples on Hexadecimal

01010001=51h, 0x51,\$51, 51₁₆

1110010 =\$72

10101110=\$AE

From Hex to decimal

\$ff= 1111 1111 =255₁₀

## Binary Codes

Binary coding is different from binary conversion

BCD code : Binary coded decimal, is used to represent each decimal digit to a 4 bit binary number,

Ex: 13 = 0001 0011 in BCD

Remember 13 = 1101 in binary

Ex: 49 = 0100 1001 in BCD

Remember that 49 = 0011 0001 in binary.

Excess-3 code

In Excess-3 0 = 0011, 1=0100, 2=0101 ,... , 9=1100

This means that we add 3 to the number then convert it to binary

We mainly use this to avoid having zeros in transmission lines.

Other coding methods ( See Page 17).

### Error detection :

Many techniques are used in order to detect if an error has occurred in the data transmitted or stored, one of these is the parity check.

The idea of the parity check is to add an extra bit to the binary number, the value of this bit depends on the number of ones in the binary number.

The parity bit is generated on transmitting end, and checked at receiving end

A parity check involves appending a bit that makes the total number of binary 1 digits in a character or word , either odd (for *odd parity*) or even (for *even parity*).

Examples:

Even parity 0000 0, 0001 1, 1111 0

Odd parity:0000 1, 0001 0, 1111 1

### Alphanumeric Codes

To represent numbers and letters we need some coding method.

First we need to know the number of symbols (letters, numbers, or other symbols)

ASCII: American standard code for information Interchange, is one of the commonly used codings  
It uses 7 bits , it can represent 127 different symbols

Ex: A = 100 0001,

a = 110 0001

1 = 011 0001

space = 010 0000

WAEL = 101 0111 100 0001 100 0101 100 1100

**EBCDIC: Extended BCD Interchange, is an 8 bit coding**

**Ex: A= 1100 0001  
1= 1111 0001  
space= 0100 0000**

75

وائل قصاص/AABU

## Summary

**MOS transistors are used as switches to implement logic functions.**

- N-type: connect to GND, turn on (with 1) to pull down to 0
- P-type: connect to +2.9V, turn on (with 0) to pull up to 1

**Basic gates: NOT, NOR, NAND**


- Logic functions are usually expressed with AND, OR, and NOT

**Properties of logic gates**

- Completeness
  - Ø can implement any truth table with AND, OR, NOT
- DeMorgan's Law
  - Ø convert AND to OR by inverting inputs and output


76

وائل قصاص/AABU

 

77

وائل قصاص/AABU

 

**First exam , Tus. 31-10-2006 from 2:00 to 2:50**

78

وائل قصاص/AABU

## Building Functions from Logic Gates

We've already seen how to implement truth tables using AND, OR, and NOT -- an example of *combinational logic*.

### *Combinational Logic Circuit*

- output depends only on the current inputs
- stateless

### *Sequential Logic Circuit*

- output depends on the sequence of inputs (previous inputs and present inputs)
- stores information (state) from past inputs

79

وائل قصاص/AABU

## Chapter 4. Combinational Circuits

A combinational circuit consists of :

- 1- Input variables.
- 2- Logic gates
- 3- Output variables

Logic gates accepts signals ( Binary signals) from inputs and generate signals to the outputs.



80

وائل قصاص/AABU



## Design Procedure

To design a combinational circuit, the following steps are used:

1. The problems in stated
2. The number of inputs and outputs are determined
3. Assigning letter symbols to each input and output
4. Building the Truth table, which defines the relationship between inputs and outputs, ( and the don't care conditions).
5. Simplifying the truth table.
6. Drawing the logic diagram.

81

وانئل قصابص /AABU

## Adders

Let us implement what we learned in the previous slide and build a combinational circuit that adds two binary numbers.

1. State the problem: Build a circuit that can add two binary numbers ( HALF ADDER)  
 $0+0=0$   
 $0+1=1$   
 $1+0=1$   
 $1+1=10$
2. Number of inputs is two , Number of outputs derived is also two.
3. Let us name the inputs as X, Y, and the outputs as S for Sum, and C for Carry_out.

82

وانئل قصابص /AABU

#### 4. Truth table

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


#### 5. Simplification:

$$C = x.y \text{ (No more simplification)}$$

$$S = x.y' + x'y$$

$$= x \oplus y$$

#### 6. Draw logic diagram

 

**Full ADDER: Build a circuit that can Add three binary numbers.**

85

وانئل قضااص/AABU

**Subtractors**  
**Half Subtractor**

86

وانئل قضااص/AABU

### Full Subtractor

X- Y - Z	BD
0 - 0 - 0 =	0 0
0 - 0 - 1 =	1 1
0 - 1 - 1 =	1 0
1 - 1 - 0 =	0 0
1 - 1 - 1 =	1 1

87

وائل قصاص/AABU

### Code Conversion

We studied before different coding techniques for numbers or alphanumeric, such as BCD, Excess_3 ,...

Let us build a combinational circuit that can convert from BCD to Excess_3.

1. BCD code and Excess_3 code are used to represent a decimal digit in binary, each code represents the decimal digit as 4 bits.
2. Let us name the BCD input variables as A,B,C,D , and the output Excess_3 variables as w,x,y,z.

88

وائل قصاص/AABU

**Truth table**

Decimal	BCD ABCD	Ex_3 wxyz
0	0000	0011
1	0001	0100
2	0010	0101
3	0011	0110
4	0100	0111
5	0101	1000
6	0110	1001
7	0111	1010
8	1000	1011
9	1001	1100

We also have don't care conditions in this example, 1010, 1011, 1100, 1101, 1110, 1111 are not accepted codes in BCD, which so can be considers as don't care.

$d(A,B,C,D)=\Sigma(10,11,12,13,14,15)$  for all outputs.

**Simplify the function for each output.**


w


x


y


z



## Example

93

وائل قصاص / AABU

## Derivation of truth table

To derive the truth table for a given logical diagram

- First label the output of each gate
- Write the function of each label, using the labels of the previous gates
- Then after putting all possible input combinations, start to find the output of each level going from input side.
- Repeat the for the next levels until you reach the output.

94

وائل قصاص / AABU

### Q 4.14

**BCD to 7 segment display.**

- 1. Build the truth table for each segment**
- 2. Minimize the function of each segment, ( use the don't care conditions)**

95

وانئل قصابص/AABU

### **MSI and LSI**

**MSI : Medium Scale Integrated circuit, < 50 gate in one IC**

**LSI : Large Scale Integrated circuit > 50 gate in one IC**

**VLSI : Very Large Scale Integrated circuit.**

**Ex.**


- **4 bit full adder**
- **BCD to 7 segment decoder**

96

وانئل قصابص/AABU



## Four-bit Adder

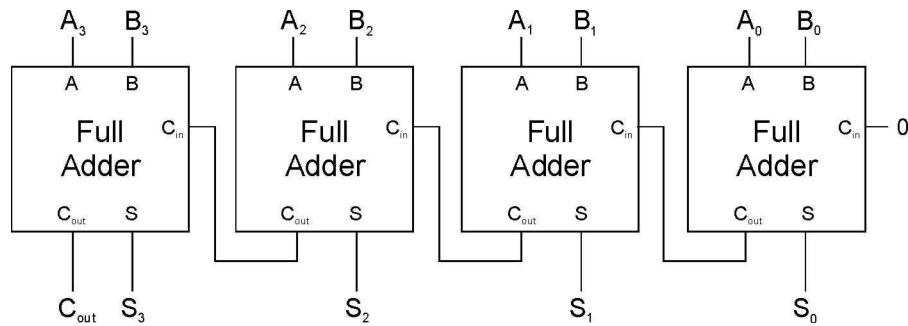

97

وائل قصاص /AABU

## Examples using MSI circuits

- Using 4 bit full adder as a BCD to Ex-3 converter
- Using the 4 bit full adder as an Ex_3 to BCD converter
- Using 4 bit full adder as a 4 bit subtractor
- Using 4 bit full adder as an adder and a subtractor

98

وائل قصاص /AABU

## Building a BCD ADDER

The BCD adder should have 9 inputs, and 5 outputs.  
Trying to build a truth table for this is not a good idea  
(number of possible states for inputs is  $2^9 = 512$ .)

We also will have many don't care states.

The other solution is to use 4bit full adders with a small combinational circuit

Things to take into consideration

1. If the sum of the 2 BCD numbers is  $\leq 9$ , no problem in the result
2. If the sum was greater than 9, it will not be in the BCD format, we need to correct the result

99

وانئل قضااص/AABU

0101      0101

0100      0111

1001=9      1100 = 12 ,

but we write 12 in BCD as 0001 0010

Another case ( worst one)

1001

1001

10010 =18

Again , in BCD 18 is 0001 1000

100

وانئل قضااص/AABU

**The solution:**

**If the resulting sum is  $>9$  we need to correct the sum by adding  $6 = 0110$**

**We have two cases**

- 1) The answer between 1010 and 1111 , with carry =0**
- 2) The carry out is 1 , which means that the sum is  $> 15$**

101

وانئل قضااص/AABU

### **4 bit Magnitude comparator**

**We need to build a combinational circuit that compares two numbers ,**

**The circuit will have 3 outputs**

**A>B**

**A<B**

**A=B**


102

وانئل قضااص/AABU
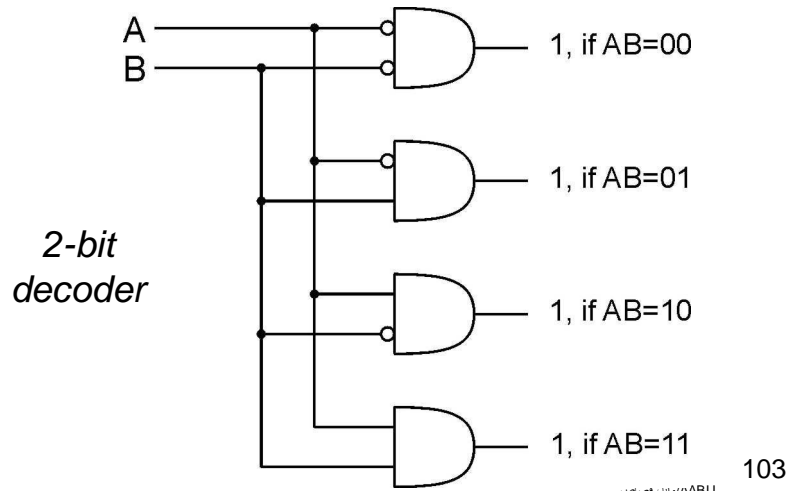
## Decoder


$n$  inputs,  $2^n$  outputs

- exactly one output is 1 for each possible input pattern



## Decoder

$n$  inputs,  $2^n$  outputs

 

104

AABU/وائل قصاص

### 3x8 Decoder


Implement combinational circuits using a decoder , OR gates

Ex. Full adder, using 3x8 decoder

105

وائل قصاص/AABU

### Inverted output decoder

 


Why we build a decoder using NAND gates?

106

وائل قصاص/AABU


### Decoder with Enable

 

107

وائل قصاص / AABU

 
### Building an 3x8 decoder using 2x4 decoders with enable



108

وائل قصاص / AABU

## 4x16 Decoder using 2x4 decoders

 


109

وائل قصاص/AABU
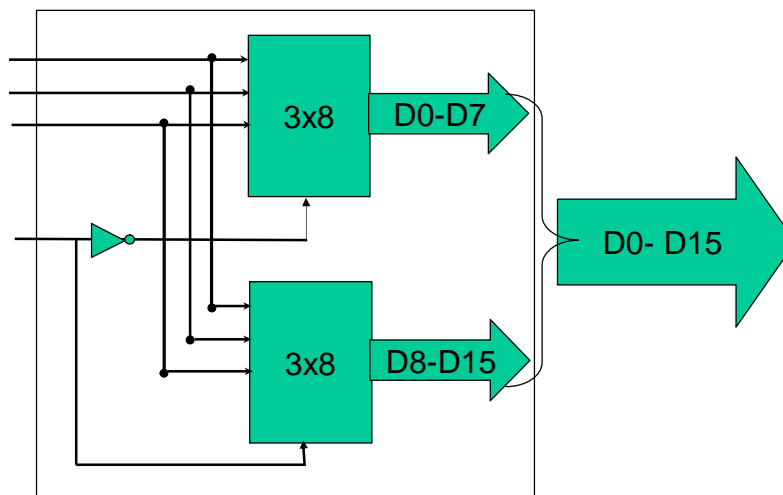
## Build larger decoders


How can we build a 4x16 decoder using 3x8 decoders



110

وائل قصاص/AABU

## Demultiplexer

 

**A demultiplexer is a combinational circuit that sends the input to the output selected by selection lines.**

**A demultiplexer can be seen as a decoder with enable.**

111

وانئل قصابص /AABU

## Encoder

**An Encoder is a digital function that produces a reverse operation for that of a decoder.**

**$2^n \times n$  encoder , has  $2^n$  inputs and n outputs**

112


وانئل قصابص /AABU


 
## Multiplexer (MUX)

$n$ -bit selector and  $2^n$  inputs, one output

- output equals one of the inputs, depending on selector




113

وائل قصاص/AABU

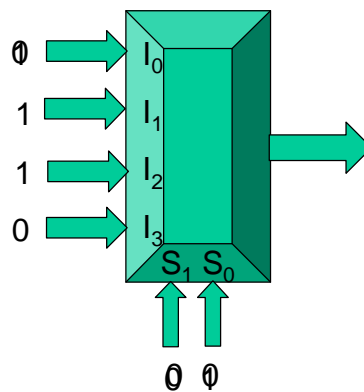
## Multiplexer (MUX)

$n$ -bit selector and  $2^n$  inputs, one output



114


وائل قصاص/AABU

 
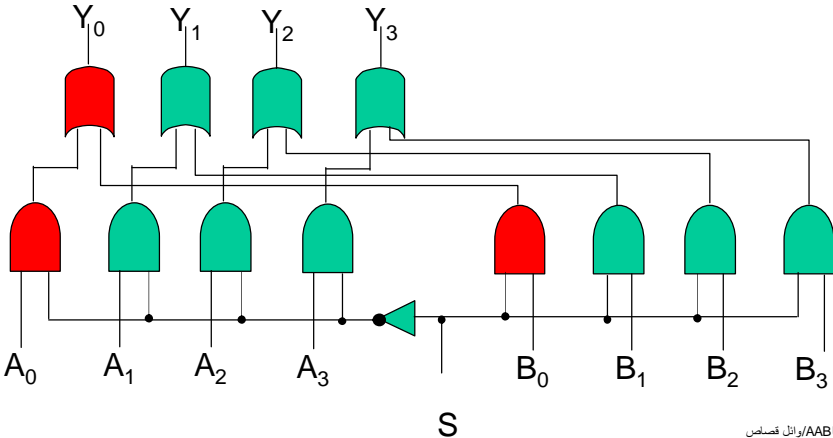
### Quadruple 2x1 Mux

If we have 2 binary numbers A & B, each is 4 bit and we need to select one of the two numbers.

We need 4 (2x1) MUXs, or a Quad 2x1 mux with one selection line .



## MUX to implement boolean functions.

We saw before how to implement a boolean function using decoders.

We can also implement this using a mux

1. If we have a function with  $n$  variables we need a MUX with  $n-1$  selection lines ( $2^{n-1}$  MUX)


2. Find the implementation table, then draw the circuit

Ex. for  $F(x,y,z)=\Sigma(1,3,5,6)$

	$I_0$	$I_1$	$I_2$	$I_3$
$X'$	0	①	2	③
$X$	4	⑤	⑥	7
	0	1	$X$	$X'$

117

وائل قصاص/AABU

 

118

وائل قصاص/AABU

**Implement the boolean function  
 $F(w,x,y,z)=\Sigma(0,1,3,4,8,9,15)$  using Multiplexer**

119  
وانئل قصابص/AABU

## **ROM**

**Types:**

**ROM**

**PROM**

**EPROM**

**EEPROM**

120  
وانئل قصابص/AABU

## HOW ROM works

It consists of a decoder and OR gates.

In general Memory has address and Data lines.

We call a ROM with  $n$  address lines and  $m$  data lines  $2^n \times m$  memory


This memory has  $2^n$  words, each word is  $m$  bits



121

روائل قصاص / AABU

8 x 4 bit Memory

 

122

روائل قصاص / AABU

From the previous discussion its clear that each output of the ROM represents a SOP

Ex.

$$D_0 = \Sigma(1,3,5,6,7)$$

$$D_1 = \Sigma(0,3,4,6,7)$$

$$D_2 =$$

$$D_3 =$$

123

وائیل قصاص / AABU

### Another example

Assume we want to build the Following Ckt that has two inputs and three outputs


$$F_0(A_1, A_0) = \Sigma(1,3)$$

$$F_1(A_1, A_0) = \Sigma(0,3)$$

$$F_2(A_1, A_0) = \Sigma(0,1,2)$$

We can build this Ckt using a 4x3 ROM =  $2^2 \times 3$  bit ROM

 This ROM is built from a decoder, OR gates



124

وائیل قصاص / AABU

**Q. What is the Data stored in this ROM?**

125  
وائیل قصاص / AABU

### **BCD to Ex.3 Converter**

**What is the size of the ROM needed?**

**What will be the data stored?**

### **BCD to 7 segment Converter**

**What is the size of the ROM needed?**

**What will be the data stored?**

126  
وائیل قصاص / AABU

## Combinational vs. Sequential

### Combinational Circuit

- always gives the same output for a given set of inputs  
Ø ex: adder always generates sum and carry, regardless of previous inputs

### Sequential Circuit

- stores information
- output depends on stored information (state) plus input  
Ø so a given input might produce different outputs, depending on the stored information
- *example*: ticket counter  
Ø advances when you push the button  
Ø output depends on previous state
- useful for building “memory” elements and “state machines”

127

وائل قصاص/AABU

## Sequential Logic

### Synchronous sequential circuits:



A system whose behavior can be defined from the knowledge of its signals at discrete instants of time.

**Asynchronous sequential circuits:** a system whose behavior depends on the order which its input signals changes at any instance of time

128

وائل قصاص/AABU



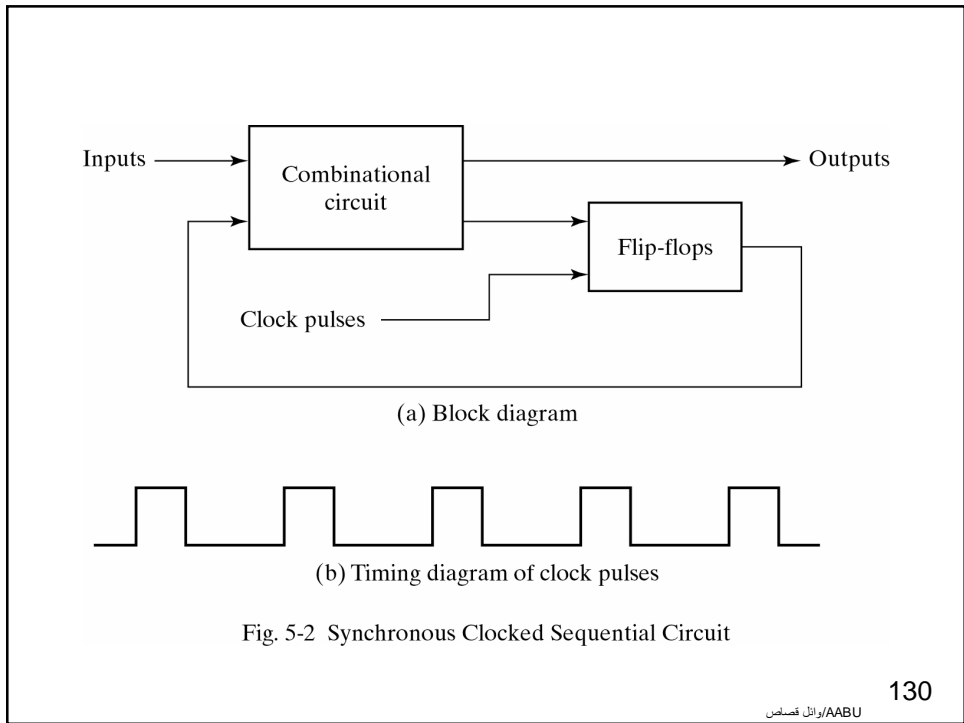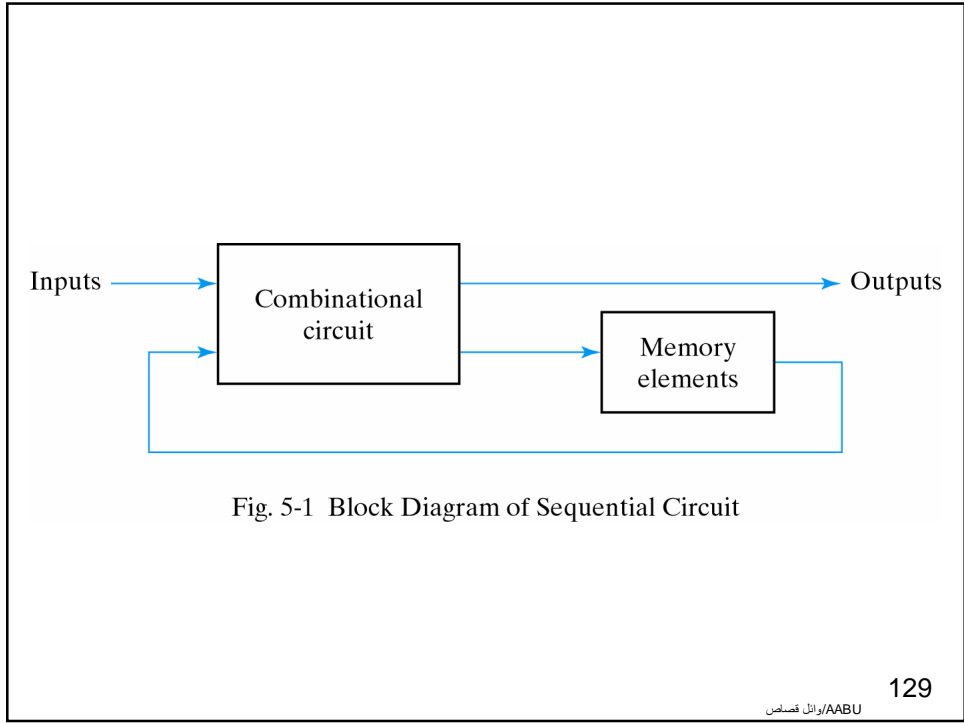

## Flip Flops

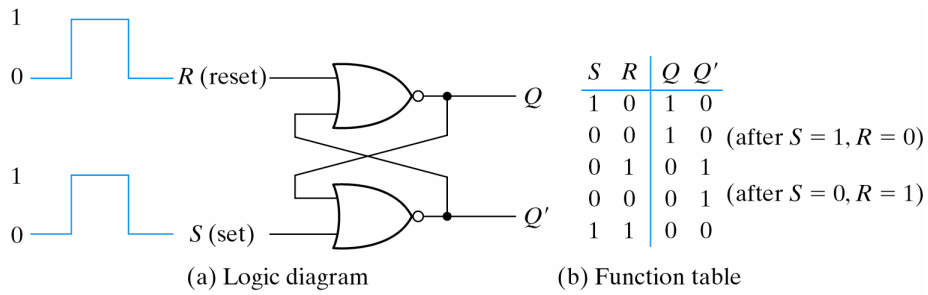


Fig. 5-3 SR Latch with NOR Gates

131

وائل قصاص/AABU


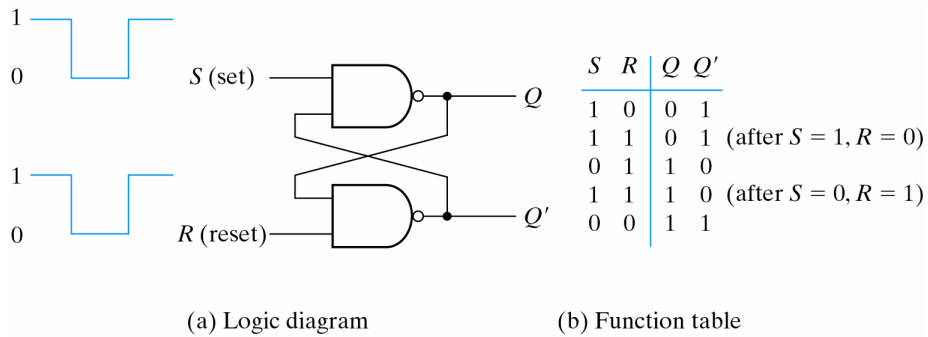
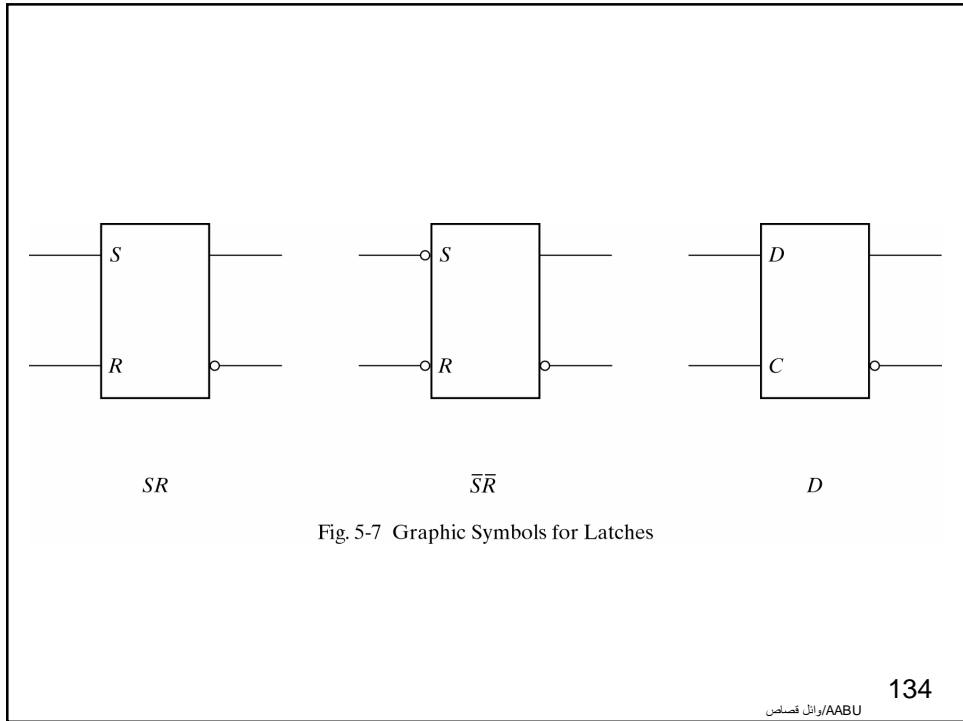


Fig. 5-4 SR Latch with NAND Gates

132


وائل قصاص/AABU

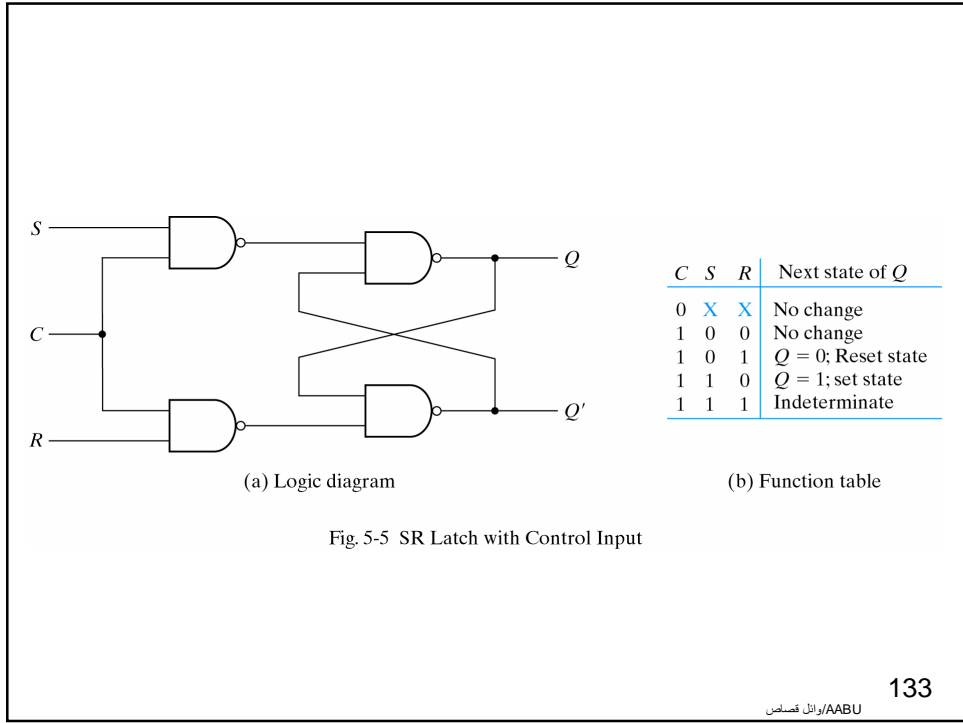
 
## R-S Latch: Simple Storage Element

R is used to “reset” or “clear” the element – set it to zero.

S is used to “set” the element – set it to one.



If both R and S are one, out could be either zero or one.


- “quiescent” state -- holds its previous value
- note: if a is 1, b is 0, and vice versa

135

وائل قصاص/AABU
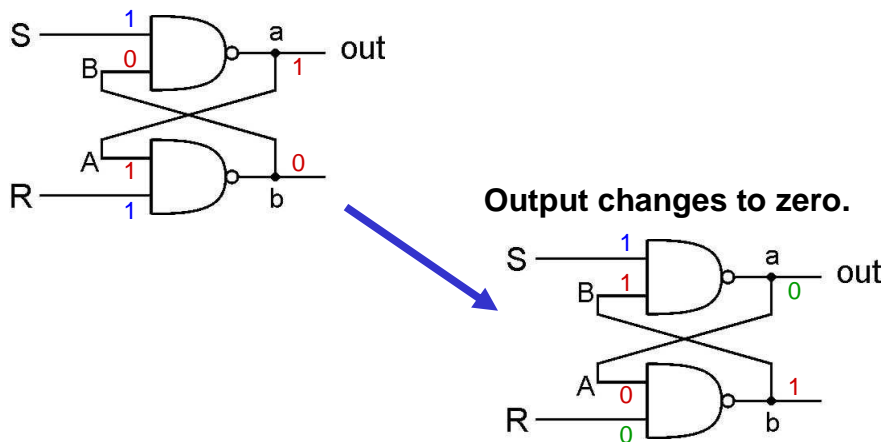
## Clearing the R-S latch

Suppose we start with output = 1, then change R to zero.



Output changes to zero.


Then set R=1 to “store” value in quiescent state.

136


وائل قصاص/AABU
 
## Setting the R-S Latch

Suppose we start with output = 0, then change S to zero.



Output changes to one.

 

Then set  $S=1$  to "store" value in quiescent state.

137

وائل قصاص/AABU

## R-S Latch Summary built by NAND

$R = S = 1$

- hold current value in latch

$S = 0, R = 1$

- set value to 1

$R = 0, S = 1$

- set value to 0

$R = S = 0$

- both outputs equal one
- final state determined by electrical properties of gates
- Don't do it!


138

وائل قصاص/AABU
 
## Gated D-Latch

Two inputs: D (data) and WE (write enable)

- when **WE = 1**, latch is set to **value of D**  
 $\emptyset S = \text{NOT}(D), R = D$
- when **WE = 0**, latch holds **previous value**  
 $\emptyset S = R = 1$



139

وائل قصاص/AABU

## Characteristic equations


Remember that the output depends on the inputs and the current state.

- First find the characteristic table
- Then derive the characteristic equation for the RS flip flop.

SR

	0	0	X	1
Q	1	0	X	1

$$Q(t+1) = S + R'Q$$

 


$Q_t$	S	R	$Q_{t+1}$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	X
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	X

140

وائل قصاص/AABU
 
## Characteristic equation for D flip flop



(a) Logic diagram

C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

(b) Function table

Fig. 5-6 D Latch

Q _t	D	Q _{t+1}
0	0	0
0	1	1
1	0	0
1	1	1

0	1
0	1

$$Q(t+1)=D$$

141


وائل قصاص/AABU

## J K flip flop

It's a refinement of RS flip flop , that defined the indeterminate states in RS.

In RS flip flop the state 11 is not allowed ,

 In JK flip flop the state 11 makes the flip flop changes (switches) its output.



142

وائل قصاص/AABU

S3S2S1S0

1010

1011

1100

1101

1110

1111

S3S2

S1S0

0	0	0	0
0	0	0	0
1	1	1	1
0	0	1	1

$S \geq 9 : \text{Cout} + S3S2 + S3S1$

143

وائل قصاص/AABU

**Problem in JK flip flop:**

- When  $J=1, K=1$  and the clock is 1,  $Q_{t+1} = Q'_t$
- Assume  $Q=1$ , it will flip to 0 then to 1 then to 0 and so on as long as the clock is 1.
- To avoid that the clock pulse (duration) must be less than the propagation delay of the Flip flop.
- But this is not a solution.
- The solution is to build a Master slave or edge triggered construction.

144

وائل قصاص/AABU



## Characteristic table and Equation

$Q_t$	J	K	$Q_{t+1}$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

		JK	
Q	0	1	1
	1	0	0

$$Q(t+1) = JQ' + K'Q$$


145

وائل قصاص/AABU
 
## T flip flop

It's a single input version of the JK Flip flop

T flip Flop has the same Problem of JK when T=1





$Q_t$	T	$Q_{t+1}$
0	0	0
0	1	1
1	0	1
1	1	0


T	Q
0	1
1	0

$$Q(t+1) = TQ' + T'Q$$

146

وائل قصاص/AABU

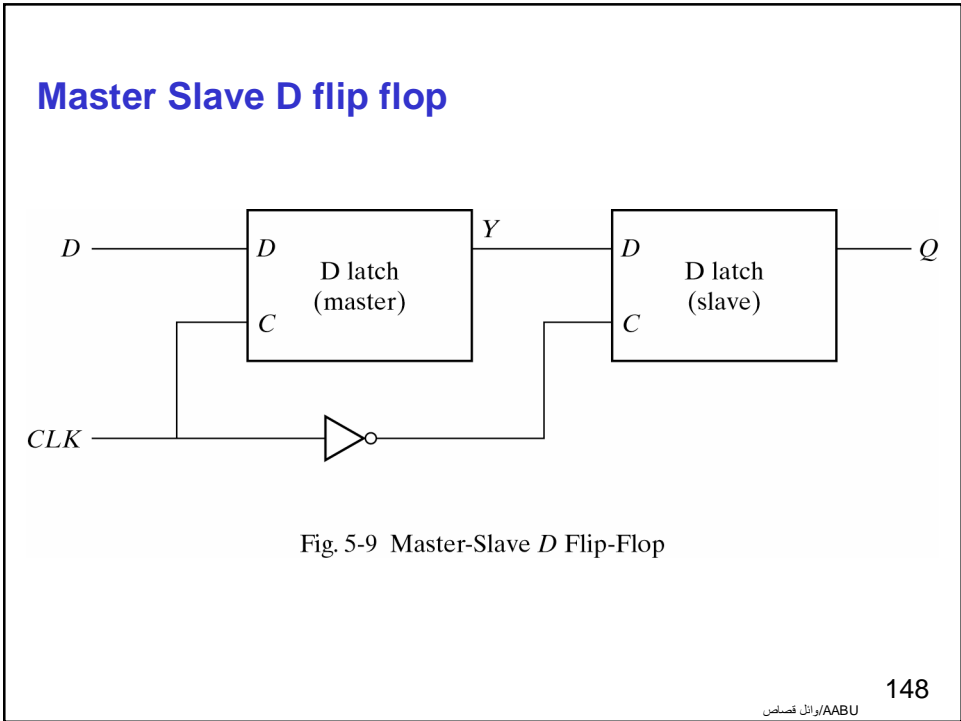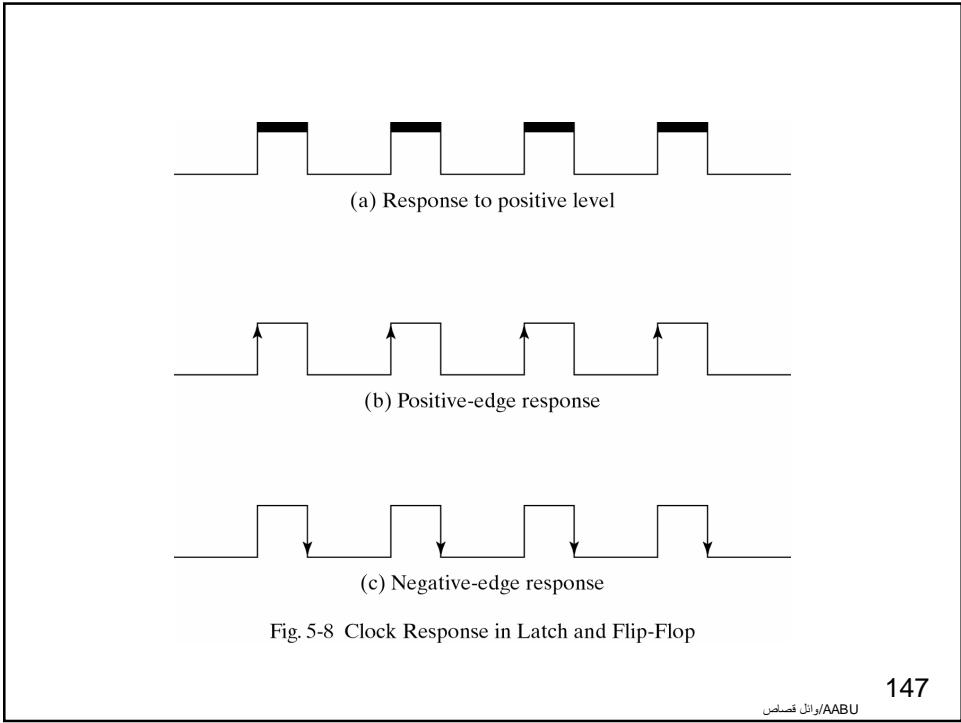


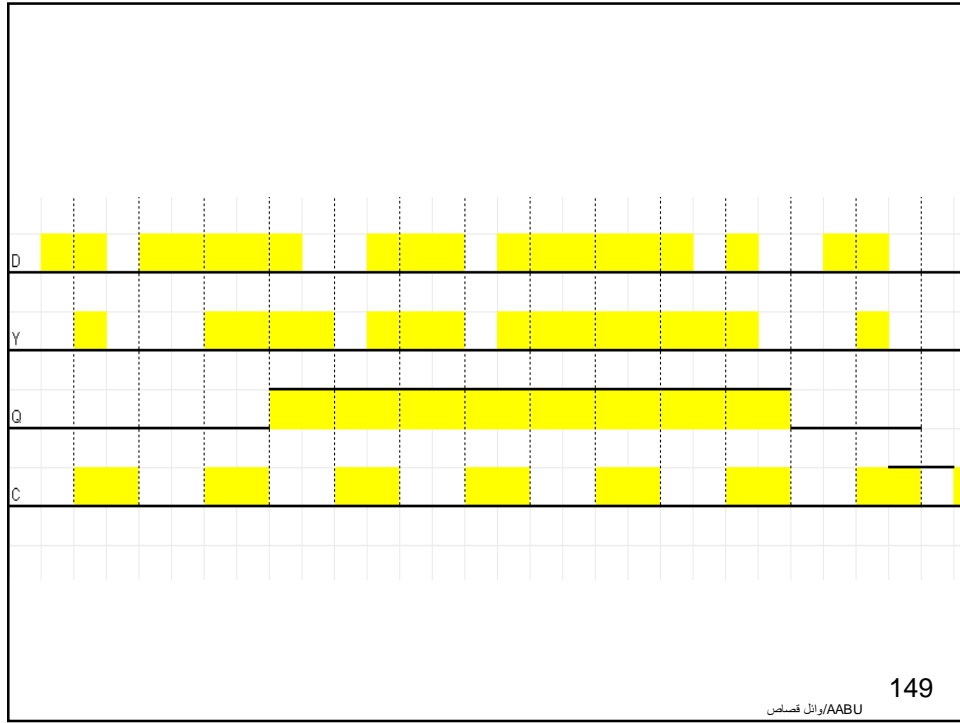

149

وانئل قضااص/AABU

### Master Slave RS flip flop

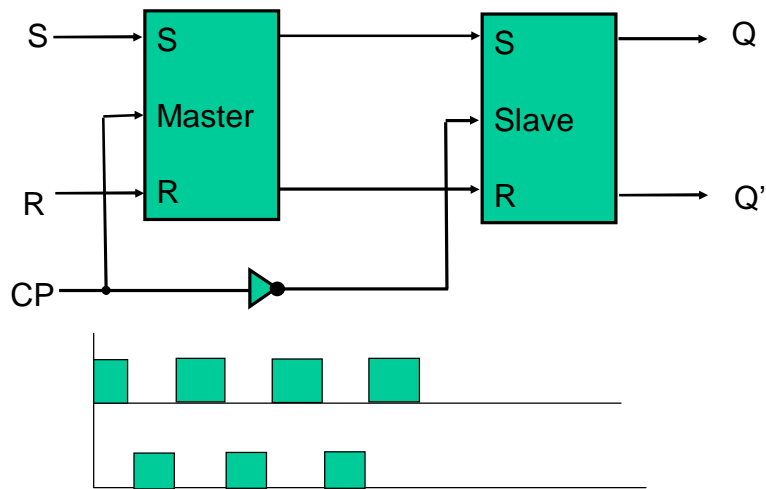

150

وانئل قضااص/AABU

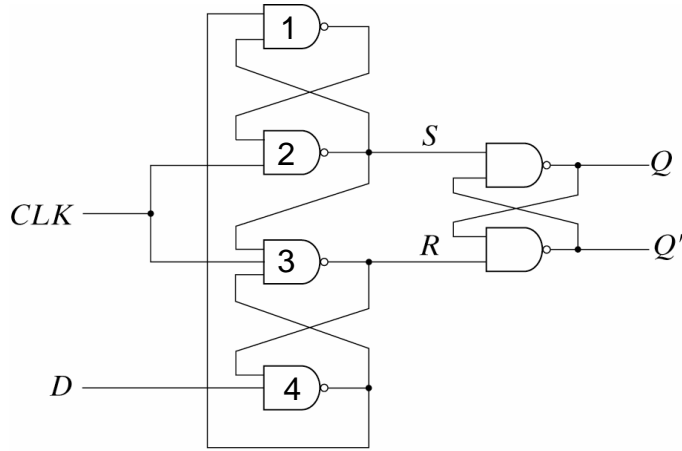


Fig. 5-10 *D*-Type Positive-Edge-Triggered Flip-Flop

151

وائل قصاص/AABU

When  $CLK = 0$  , gates 2,3 are not working, gate 2=1.  
 gate3=1  $\Rightarrow R=1, S=1$   
 $\Rightarrow$  No change in the output.  
 If  $D=0$ ; Gate 4=1, Gate1 =0.  
 If  $D=1$ ; Gate 4=0, Gate1 =1.

152

وائل قصاص/AABU

**IF D=0è Gate1=0,Gate4=1,Gate2=1,Gate3=1;  
and CLK goes to 1**

**Gate 4=1, Gate 3=0, Gate1=0;Gate 2=1;**

**After the CLK being 1, if D changed to 1, this will not affect  
on Gate 4 , nor any other gates.**

153

وائل قصاص/AABU



**IF D=1è Gate1=1,Gate4=0,Gate2=1,Gate3=1;  
and CLK goes to 1**


**Gate 4=0, Gate 3=1, Gate1=1;Gate 2=0;**

**After the CLK being 1, if D changed to 0, Gate 4 =1 , other  
gates will not affect by this change.**

154

وائل قصاص/AABU

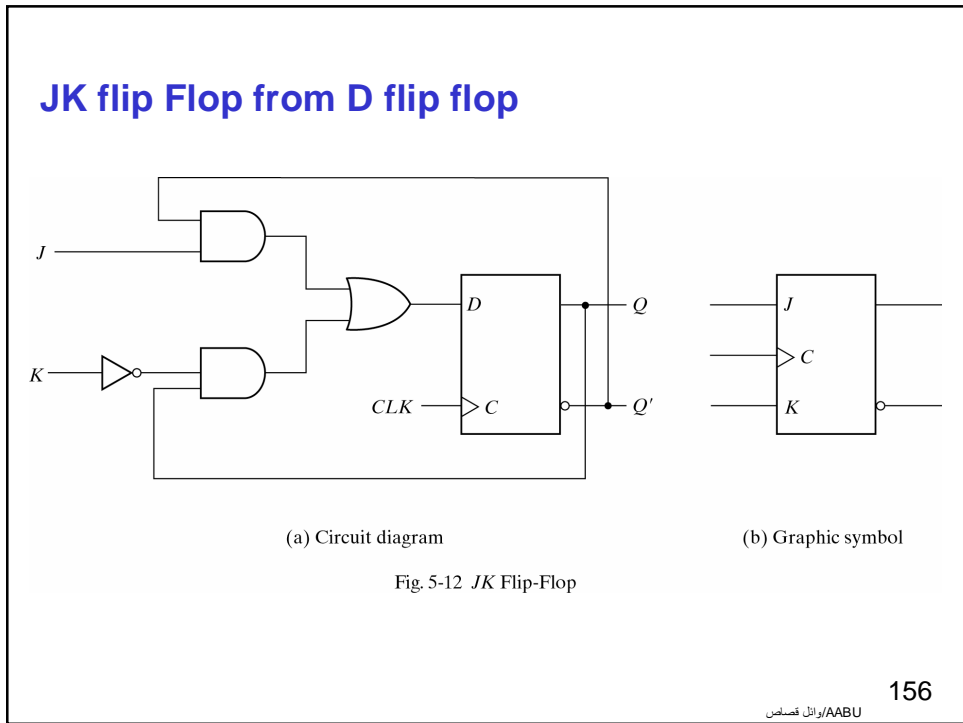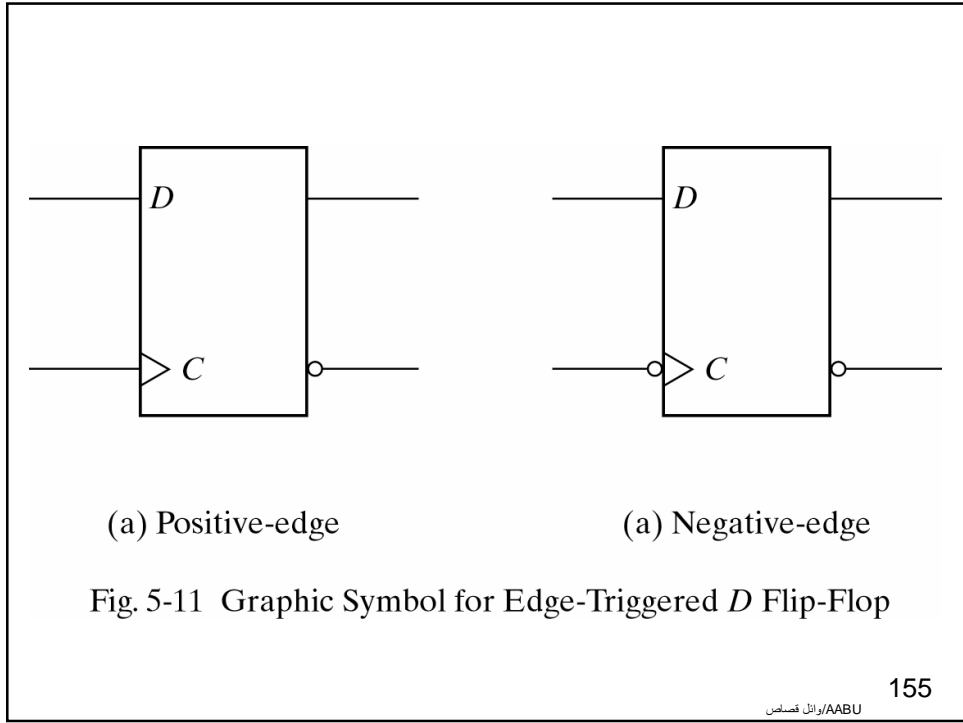

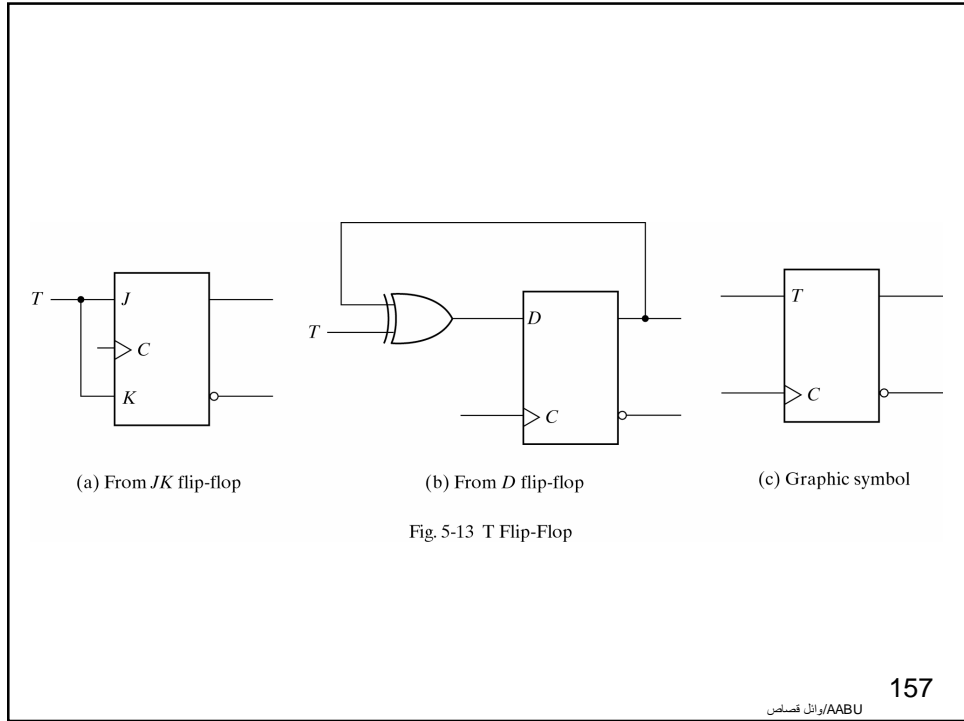

### Analysis of sequential circuit

The behavior of a seq. ckt is determined form


- a) Inputs
- b) Outputs
- c) States of its flip flop

Both outputs and next state are function of input and present state.

From a seq. ckt diagram , we will find the

- a) state table
- b) State diagram

## Example

 

159

وائل قصاص / AABU

## State Table

Present State	Next state		Output	
	X=0	X=1	X=0	X=1
AB	AB	AB	Y	Y
00	00	01	0	0
01	11	01	0	0
10	10	00	0	1
11	10	11	0	0


160

وائل قصاص / AABU


 
## State diagram

The state table can be represented graphically using the state diagram. Transition from a state to state is shown as arrow labeled with two values (Input/output)



161

وائیل قصاص / AABU

## State equation

State equation (or application equation) is an expression that shows the relation for the next state of each flip flop as a function of the present state and the inputs,

Method 1: using the characteristic equation of the flip flop

$$A(t+1) = S + R'Q$$

$$= X'.B + (X.B')'.A$$

$$= X'.B + (X' + B).A$$

$$= X'.B + X'.A + A.B$$

$$B(t+1) = S + R'Q$$

$$= X.A' + (X'.A)'.B$$

$$= X.A' + X.B + A'.B$$

162

وائیل قصاص / AABU

## State equation

Method 2:

From the state table.

$$\begin{aligned}A(t+1) &= (A'B+AB'+AB).X' + ABX \\ &= A'BX'+AB'X'+ABX' + ABX \\ &= BX'+AX'+AB\end{aligned}$$

## 6.7 Design procedure

1. Build the state diagram
2. Build the state table
3. Assign binary values for each state
4. Determine the number of flip flops needed and assign a symbol for each flip flop
5. Choose the type of flip flop to be used (we will use JK)
6. From the state table derive the excitation and output tables
7. Simplify the flip flop functions
8. Draw the logic diagram

The following formulas for JK flip flop inputs will help us

$Q_t$   $Q_{t+1}$

0 to 0 J=0, K=X ( don't care)

0 to 1 J=1, K=X

1 to 0 J=X, K=1

1 to 1 J=X, K=0

165

وائل قصاص/AABU

### Excitation tables for Flip Flops

$Q_t$	$Q_{t+1}$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

RS

$Q_t$	$Q_{t+1}$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

JK

$Q_t$	$Q_{t+1}$	D
0	0	0
0	1	1
1	0	0
1	1	1

D

$Q_t$	$Q_{t+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0


T

166

وائل قصاص/AABU
 
### Example 1

Design a circuit that works as a counter from 0 to 3 if the input x is 1 and stay in the same state if x is 0



167

وائل قصاص/AABU

### Example 0

Design a counter that counts from 3 down to 0 one step on each clock

168

وائل قصاص/AABU

### State table

	X=0	X=1
AB	AB	AB
00	00	01
01	01	10
10	10	11
11	11	00

We have 4 states so we need 2 flip flops

### Excitation table

A B X	Next state	flip flop inputs			
	A B	JA	KA	JB	KB
0 0 0	0 0	0	X	0	X
0 0 1	0 1	0	X	1	X
0 1 0	0 1	0	X	X	0
0 1 1	1 0	1	X	X	1
1 0 0	1 0	X	0	0	X
1 0 1	1 1	X	0	1	X
1 1 0	1 1	X	0	X	0
1 1 1	0 0	X	1	X	1

Now we need to simplify the equation of each flip flop input

0	0	1	0
x	x	x	X

$$JA=Bx$$

0	1	x	X
0	1	x	x

$$JB=x$$

x	x	x	X
0	0	1	0

$$KA=Bx$$

x	x	1	0
x	x	1	0

$$KB=x$$

171

وائل قصاص/AABU

### Example 2

Design a circuit that works as a down counter from 3 down to 0 if the input  $x$  is 1 and stay in the same state if  $x$  is 0


172

وائل قصاص/AABU

### Example 3

Design a sequential Ckt that generate the following sequence 000, 001, 010,100 , using JK flip flops

This circuit has 4 states

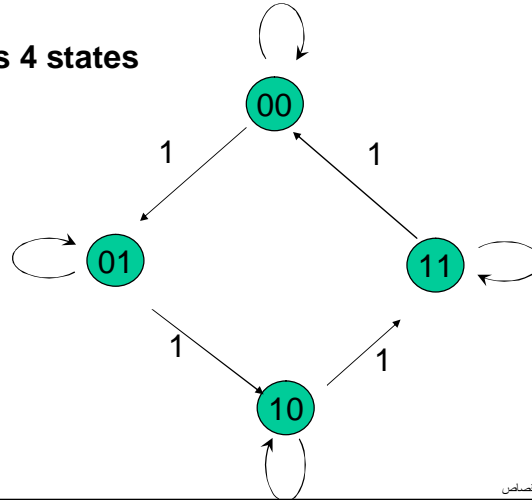

173

وائل قصاص/AABU

### Example 4

Repeat example 1 using RS flip flop

1) How RS Flip flop works

0 to 0 S=0, R=X ( don't care)

0 to 1 S=1, R=0

1 to 0 S=0, R=1

1 to 1 S=X, R=0

2) Build the Excitation table, then simplify the equations that represents R and S for each flip flop.

174

وائل قصاص/AABU

### Excitation table

A B X	Next state	flip flop inputs			
	A B	SA	RA	SB	RB
0 0 0	0 0	0	X	0	X
0 0 1	0 1	0	X	1	0
0 1 0	0 1	0	X	X	0
0 1 1	1 0	1	0	0	1
1 0 0	1 0	X	0	0	X
1 0 1	1 1	X	0	1	0
1 1 0	1 1	X	0	X	0
1 1 1	0 0	0	1	0	1

Now we need to simplify the equation of each flip flop input

175

وائل قصاص/AABU

0	0	1	0
X	X	0	X

SA=

X	X	0	X
0	0	1	0

RA=

0	1	0	X
0	1	0	X

SB=

x	0	1	0
x	0	1	0

RB=


176

وائل قصاص/AABU


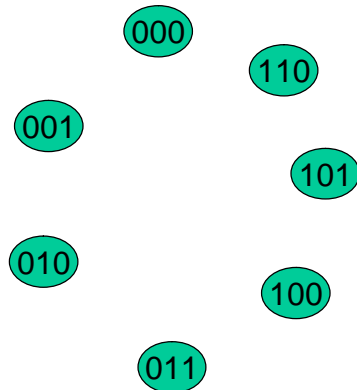
### Example 5

Design an up_down counter that counts from 0 to 6, depending on the input value, if  $x=0$  it counts down, if 1 it counts up




177

وائل قصاص/AABU

We have a small problem here.

What if the counter started with 111 ?

 We need to move it to one of the valid states,  
To 000 for example




178

وائل قصاص/AABU
 
### Non-Standard Counters

- Counters are sometimes defined that count in an order other than standard numerical order.
- The state machine below is for a *gray code* counter in which one bit changes at a time.



$q_2 \backslash q_1q_0$	00	01	11	10
$q_0$ 0	1	1	0	0
1	0	0	1	1

$q_2 \backslash q_1q_0$	00	01	11	10
$q_1$ 0	0	1	1	1
1	0	0	0	1

$q_2 \backslash q_1q_0$	00	01	11	10
$q_2$ 0	0	0	0	1
1	0	1	1	1

179

وائل قصاص/AABU

### 3 bit binary counter


 
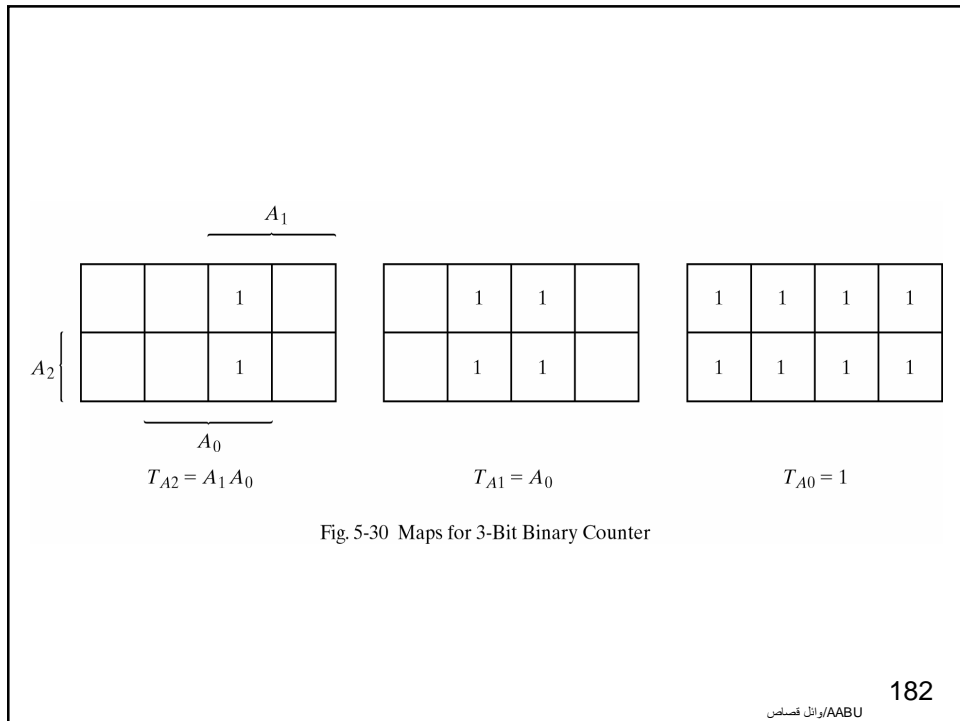


Fig. 5-29 State Diagram of 3-Bit Binary Counter

180



وائل قصاص/AABU

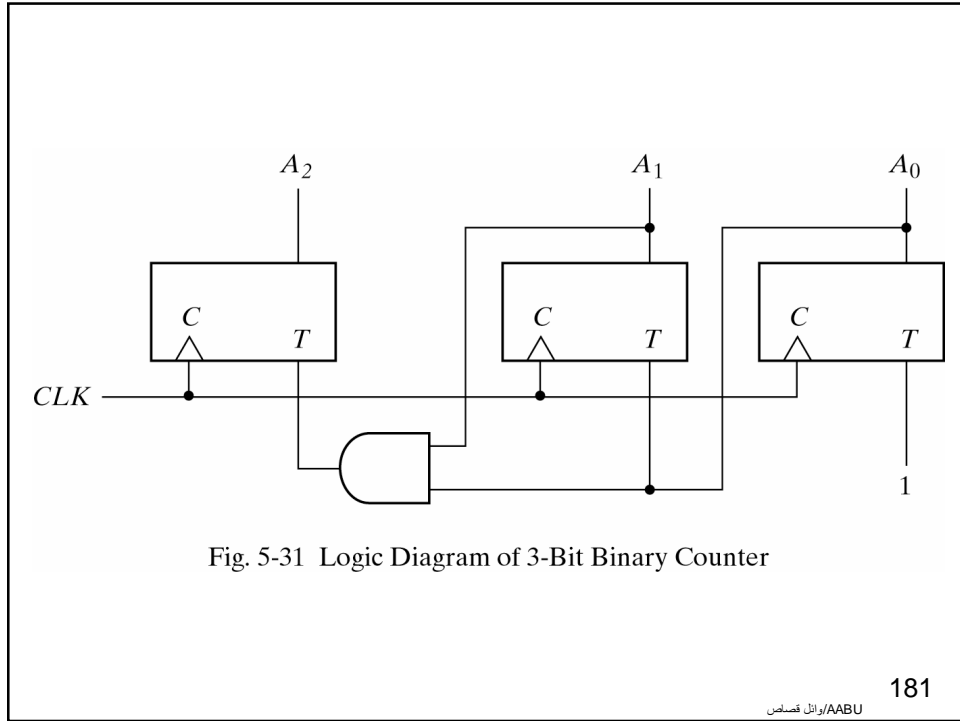

## Complete Example
  
### A blinking traffic sign


- No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)
- When the input is 0, No lights on



183

وائل قصاص/AABU


## Traffic Sign State Diagram

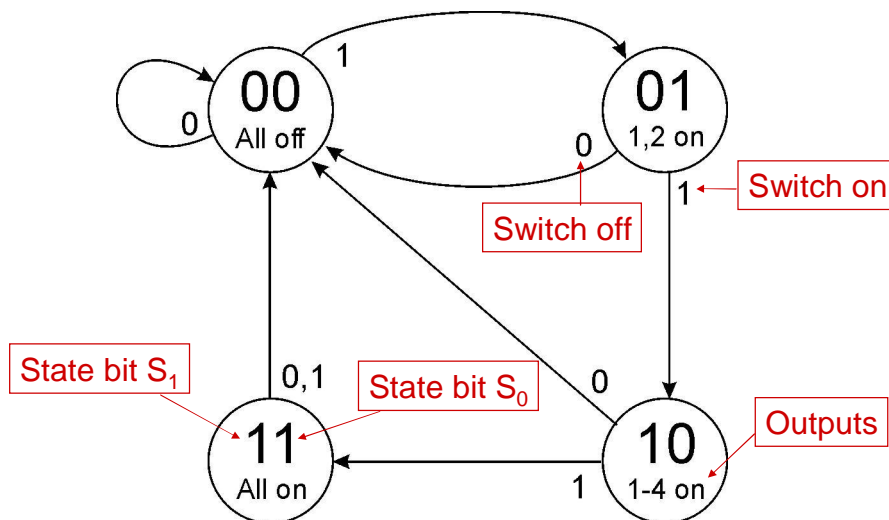

Transition on each clock cycle.

184

وائل قصاص/AABU

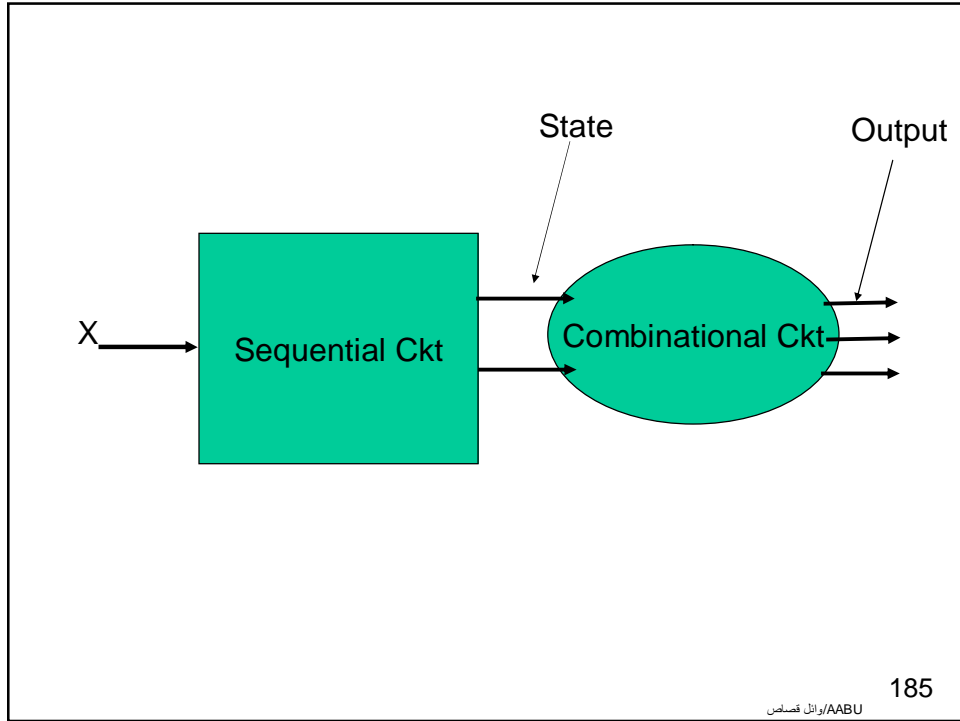

### Traffic Sign Truth Tables

Outputs  
(depend only on state:  $S_1S_0$ )

$S_1$	$S_0$	Z	Y	X
0	0	0	0	0
0	1	1	0	0
1	0	1	1	0
1	1	1	1	1

Lights 1 and 2 → Z  
 Lights 3 and 4 → Y  
 Light 5 → X

Next State:  $S_1'S_0'$   
(depend on state and input)

In	$S_1$	$S_0$	$S_1'$	$S_0'$
0	X	X	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

Switch → In

Whenever In=0, next state is 00.

186

وائل قصاص / AABU

## 2 input Sequential Ckts

Q. Build a counter that counts from 0 to 3, this counter has two inputs X,Y,

XY

00 Reset the counter ( go to state 00)

01 Count forward

10 Counts backward


11 No change

187

وانئل قصابص/AABU

We have 4 states  $\Rightarrow$  we need two flip flops

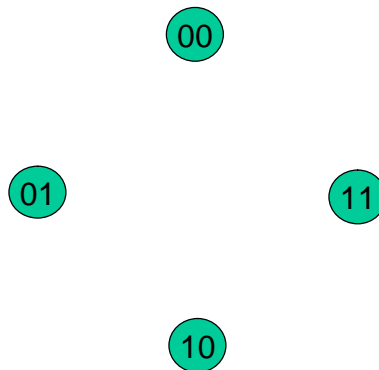We have 2 inputs  $\Rightarrow$  each state has 4 transitions



188

وانئل قصابص/AABU

### State table

Present state A B	Next state			
	XY=00 A B	XY=01 A B	XY=10 A B	XY=11 A B
0 0				
0 1				
1 0				
1 1				

189

وانئل قصابص /AABU

### Excitation table

XYAB	AB	TA	TB
0000			
0001			
0010			
0011			
0100			
0101			
0110			
0111			
1000			
1001			
1010			
1011			
1100			
1101			
1110			
1111			



190

وانئل قصابص /AABU


## Chapter 7

### Registers, Counters, and Memory units
 
### Gated D-Latch

Two inputs: D (data) and WE (write enable)

- when **WE = 1**, latch is set to **value of D**  
 $\emptyset S = \text{NOT}(D), R = D$
- when **WE = 0**, latch holds **previous value**  
 $\emptyset S = R = 1$





 
## Register

A register stores a multi-bit value.


- We use a collection of D-latches, all controlled by a common WE.
- When WE=1, n-bit value D is written to register.



193



وائل قصاص/AABU

## 4 bit register

 


194


وائل قصاص/AABU

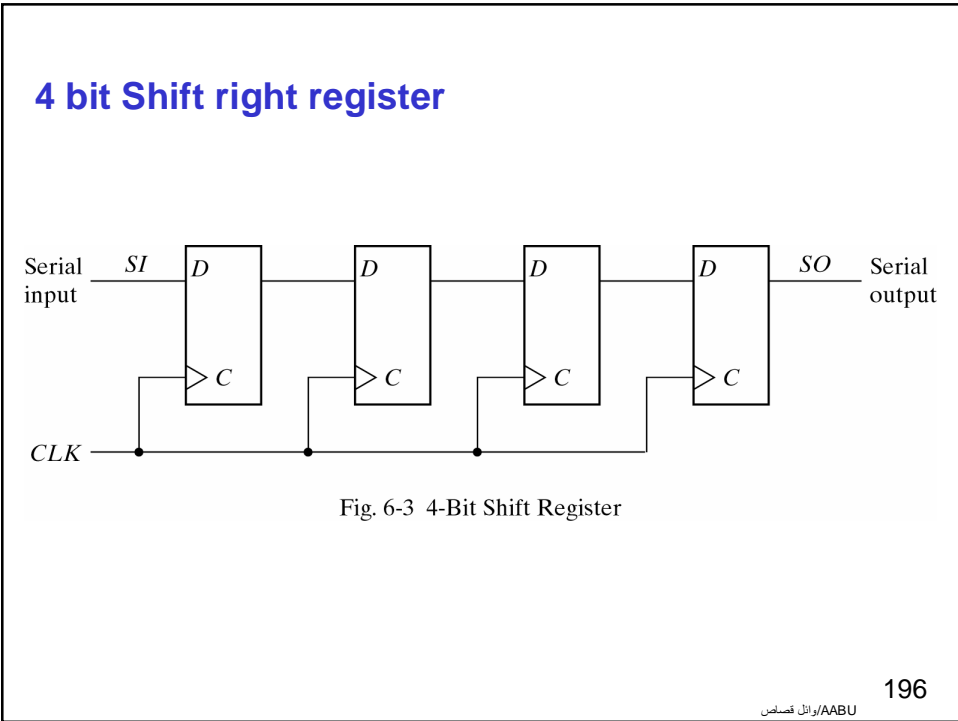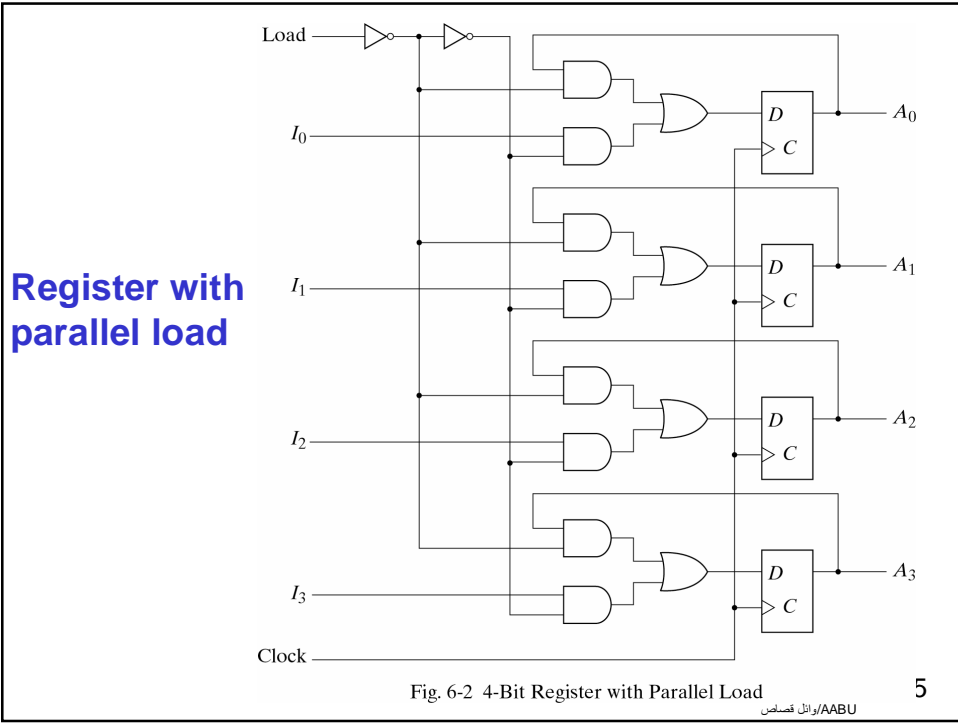

## Serial Transfer

 

(a) Block diagram

 

(b) Timing diagram

Fig. 6-4 Serial Transfer from Register A to register B

197

وائل قصاص/AABU



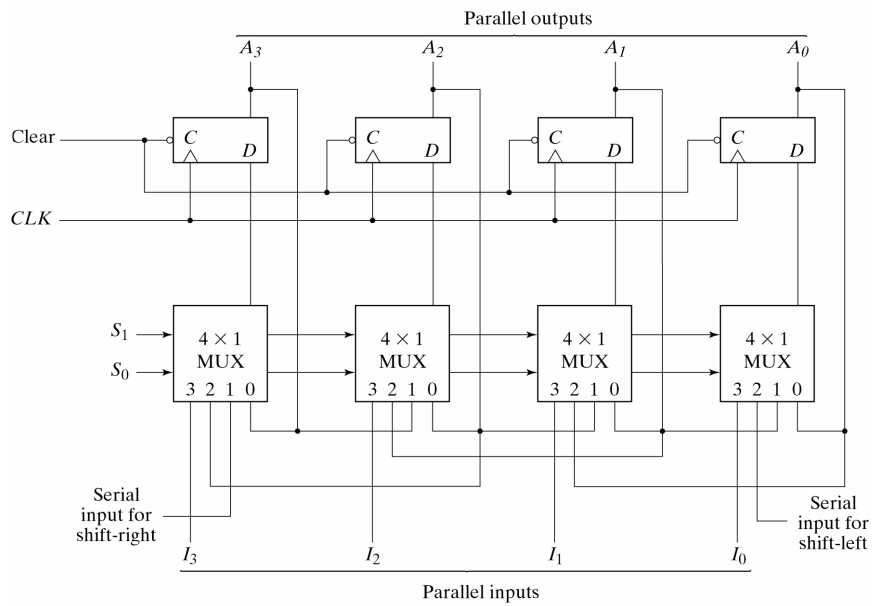


Fig. 6-7 4-Bit Universal Shift Register

198

وائل قصاص/AABU

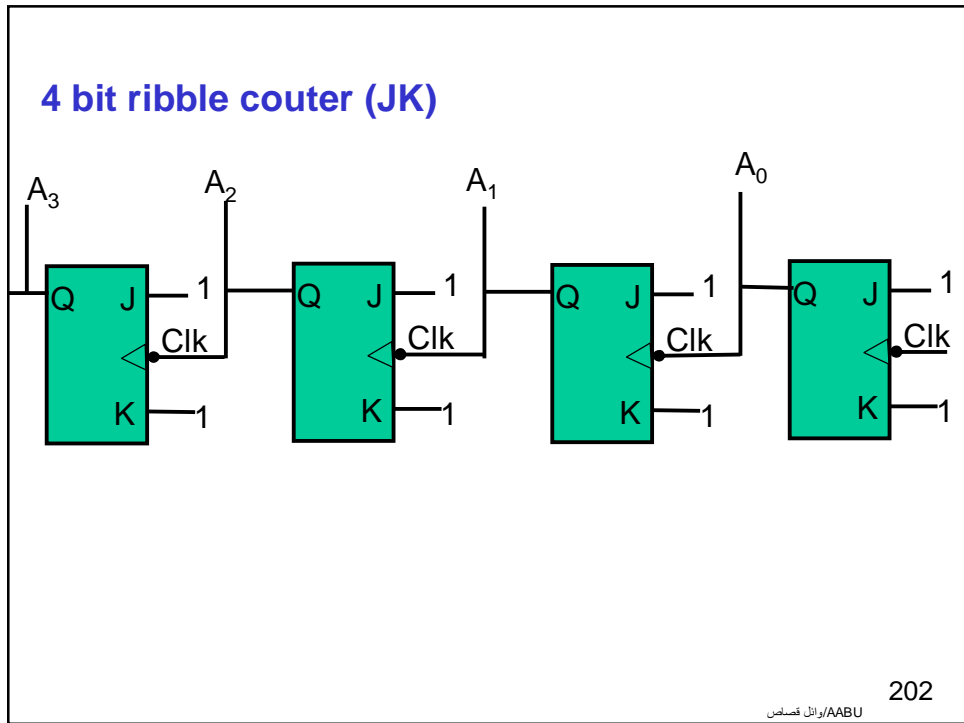

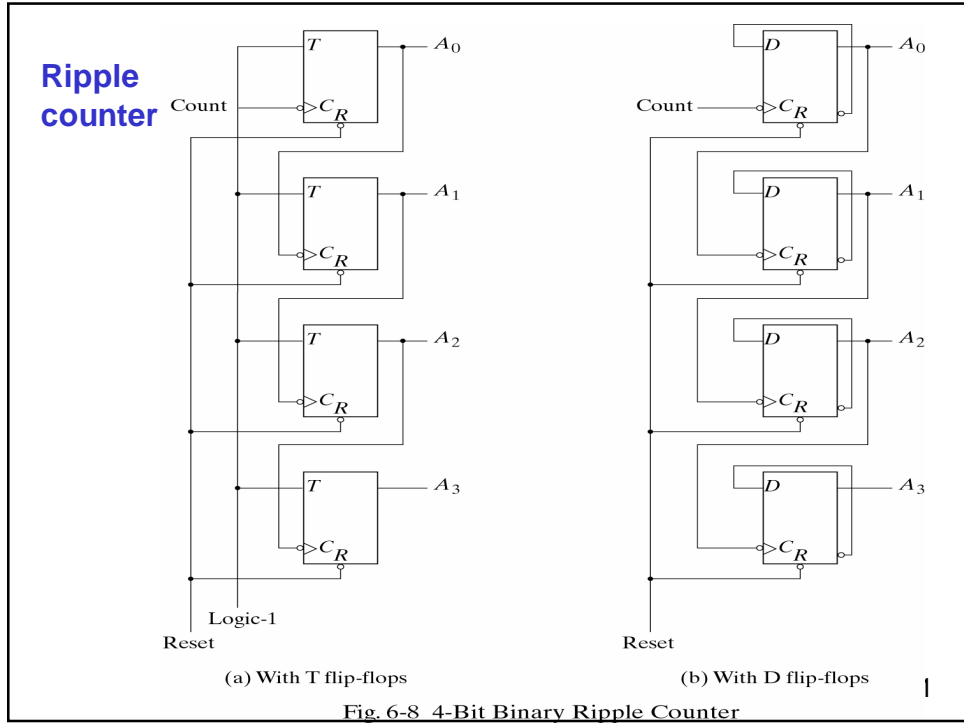

### Decimal counter

 


Fig. 6-9 State Diagram of a Decimal BCD-Counter

203

وائل قصاص/AABU

### BCD Ripple counter

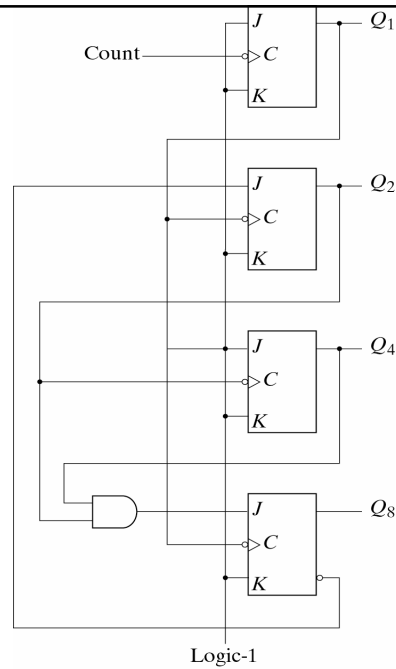


Fig. 6-10 BCD Ripple Counter

204


وائل قصاص/AABU

- In BCD counter the first digit flips with the clock,
- The second digit flips depending on the first digit a clock if the number is less than 8, since J is connected to  $Q_8'$
- When  $Q_8$  becomes 1, J will be 0, this will clear  $Q_2$ .
- BUT this will take effect only after  $Q_0$  goes from 1 to 0.
- What about J8

205

وائل قصاص / AABU

### MSI 4 bit counter with Parallel load

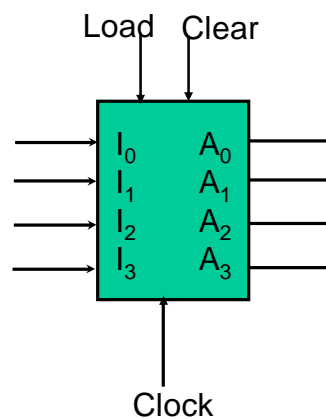


206

وائل قصاص / AABU
 
## Using an MSI Binary counter , Build a BCD counter

- As you know, BCD counter goes to 0 after 9.
- All what we want to do is to load 0 if the counter value is 9



207

وائل قصاص / AABU

## Build a counter that counts from 0 to 6

208

وائل قصاص / AABU



**Build a counter that counts from 5 to 13**

209  
وائل قصاص / AABU

**Johnson counter**


**Self read.**

**Required for the exam.**

210  
وائل قصاص / AABU
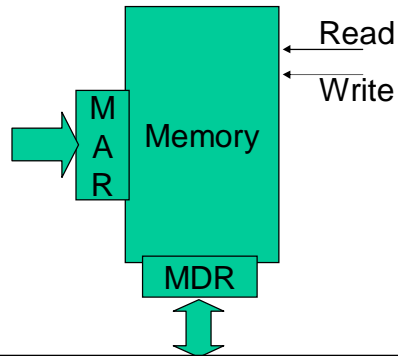
## Memory Unit



- A memory unit stores binary information in groups called *words*. Each is  $n$  bits.
- Memory size is the number of locations (words) that a memory have.
- A memory word ( which contains binary numbers) is used to represent an Instruction, Number, Character,...
- MAR
- MDR



211

وائل قصاص/AABU

## Binary Cell & RAM

  

212

وائل قصاص/AABU

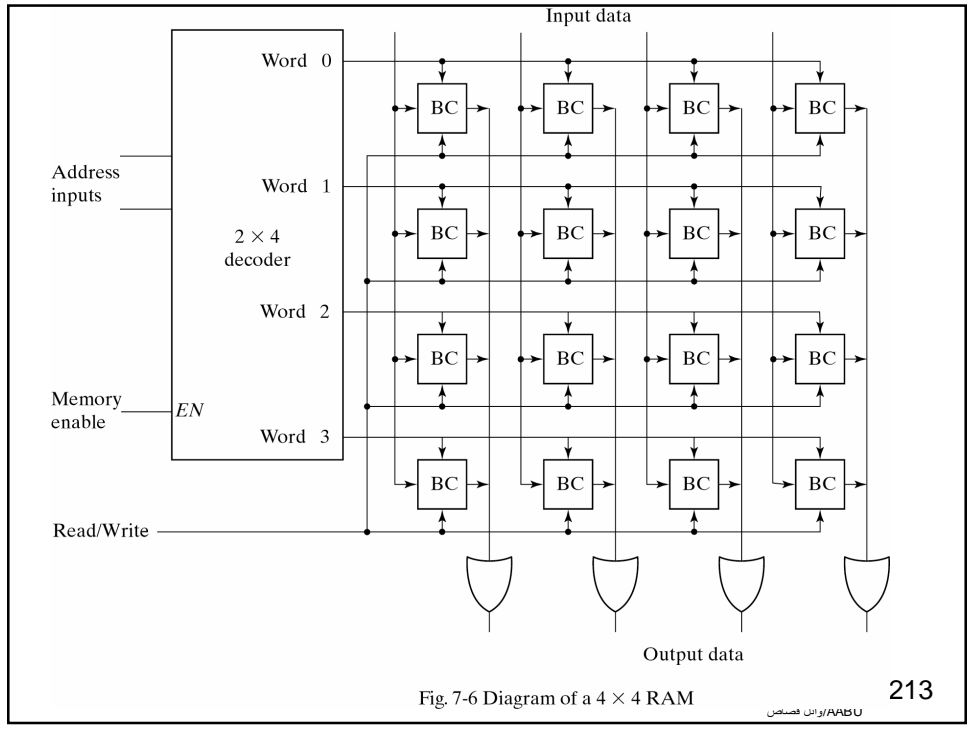


Fig. 7-6 Diagram of a  $4 \times 4$  RAM